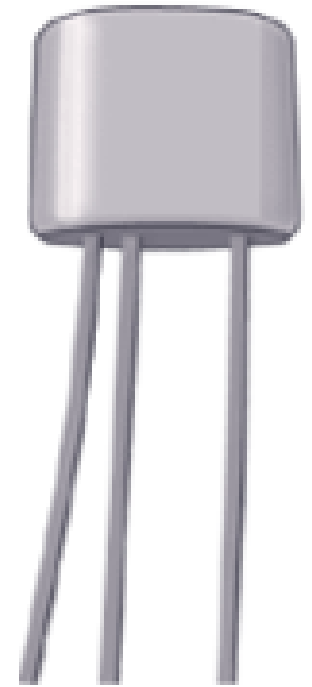


Transistors

- What is a Transistor?
- History
- Types
- Characteristics
- Applications

What is a Transistor?

- Semiconductors: ability to change from conductor to insulator
- Can either allow current or prohibit current to flow
- Useful as a switch, but also as an amplifier
- Essential part of many technological advances




A Brief History

- Guglielmo Marconi invents radio in 1895
- Problem: For long distance travel, signal must be amplified
- Lee De Forest improves on Fleming's original vacuum tube to amplify signals
- Made use of third electrode
- Too bulky for most applications

The Transistor is Born

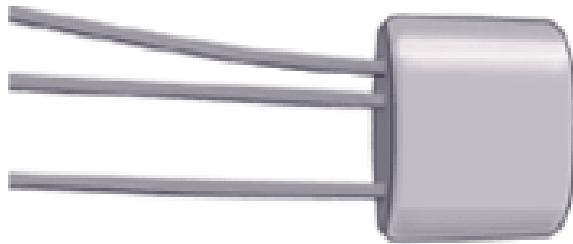- Bell Labs (1947): Bardeen, Brattain, and Shockley
- Originally made of germanium
- Current transistors made of doped silicon





How Transistors Work

- Doping: adding small amounts of other elements to create additional protons or electrons
- P-Type: dopants lack a fourth valence electron (Boron, Aluminum)
- N-Type: dopants have an additional (5th) valence electron (Phosphorus, Arsenic)
- Importance: Current only flows from P to N

Diodes and Bias

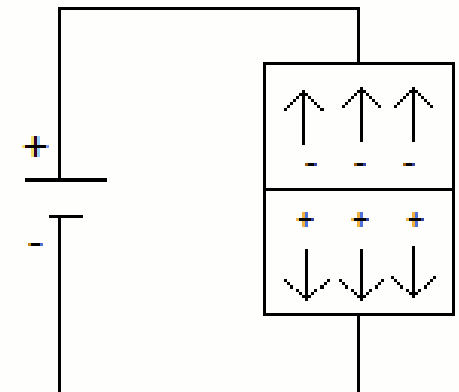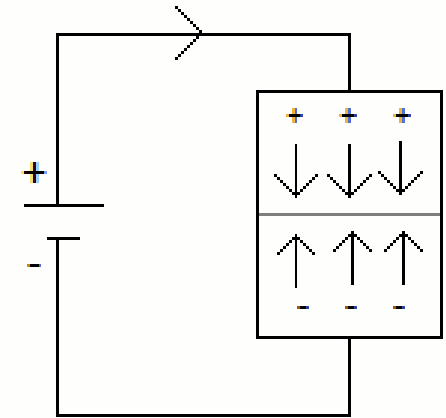
- Diode: simple P-N junction.
- Forward Bias: allows current to flow from P to N.
- Reverse Bias: no current allowed to flow from N to P.
- Breakdown Voltage: sufficient N to P voltage of a Zener Diode will allow for current to flow in this direction.




Bipolar Junction Transistor (BJT)

- 3 adjacent regions of doped Si (each connected to a lead):
 - Base. (thin layer, less doped).
 - Collector.
 - Emitter.
- 2 types of BJT:
 - npn.
 - pnp.
- Most common: npn (focus on it).

Developed by
Shockley (1949)

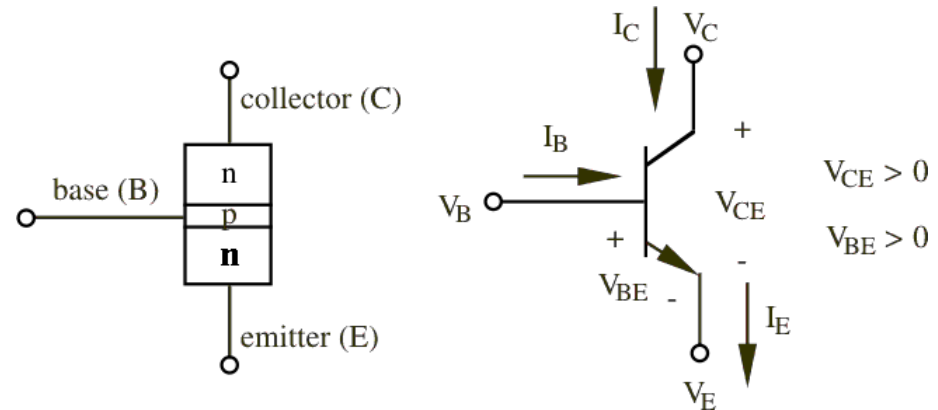

npn bipolar junction transistor

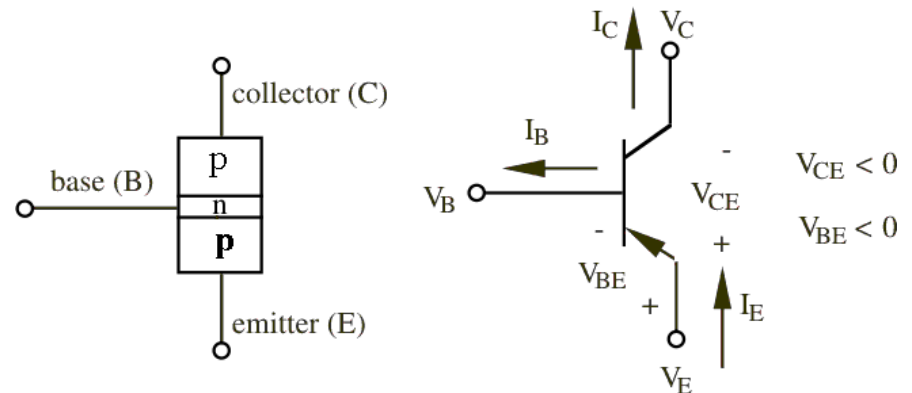

pnp bipolar junction transistor

BJT npn Transistor

- 1 thin layer of p-type, sandwiched between 2 layers of n-type.
- N-type of emitter: more heavily doped than collector.
- With $V_C > V_B > V_E$:
 - Base-Emitter junction forward biased, Base-Collector reverse biased.
 - Electrons diffuse from Emitter to Base (from n to p).
 - There's a depletion layer on the Base-Collector junction → no flow of e⁻ allowed.
 - **BUT** the Base is thin and Emitter region is n⁺ (heavily doped) → electrons have enough momentum to cross the Base into the Collector.
 - The small base current I_B controls a large current I_C



$$V_C > V_B > V_E$$

$$I_E = I_C + I_B$$

$$V_{BE} = V_B - V_E$$

$$V_{CE} = V_C - V_E$$

$$I_C = \beta I_B$$

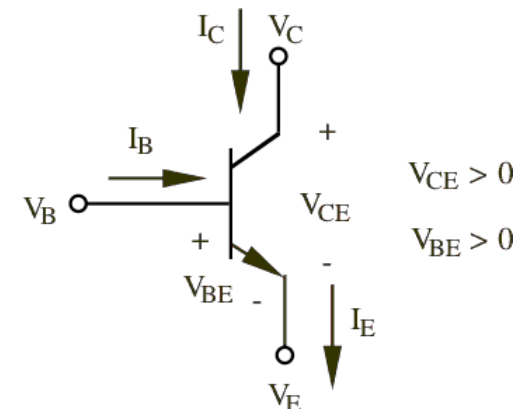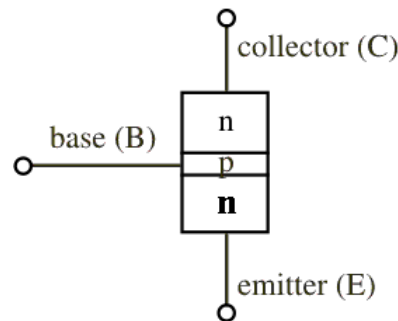

BJT characteristics

- Current Gain:
 - α is the fraction of electrons that diffuse across the narrow Base region
 - $1 - \alpha$ is the fraction of electrons that recombine with holes in the Base region to create base current
- The current Gain is expressed in terms of the β (beta) of the transistor (often called h_{fe} by manufacturers).
- β (beta) is Temperature and Voltage dependent.
- It can vary a lot among transistors (common values for signal BJT: 20 - 200).

$$I_C = \alpha I_E$$

$$I_B = (1 - \alpha) I_E$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

npn Common Emitter circuit

- Emitter is grounded.
- Base-Emitter starts to conduct with $V_{BE}=0.6V$, I_C flows and it's $I_C=\beta \cdot I_B$.
- Increasing I_B , V_{BE} slowly increases to $0.7V$ but I_C rises exponentially.
- As I_C rises, voltage drop across R_C increases and V_{CE} drops toward ground. (transistor in saturation, no more linear relation between I_C and I_B)

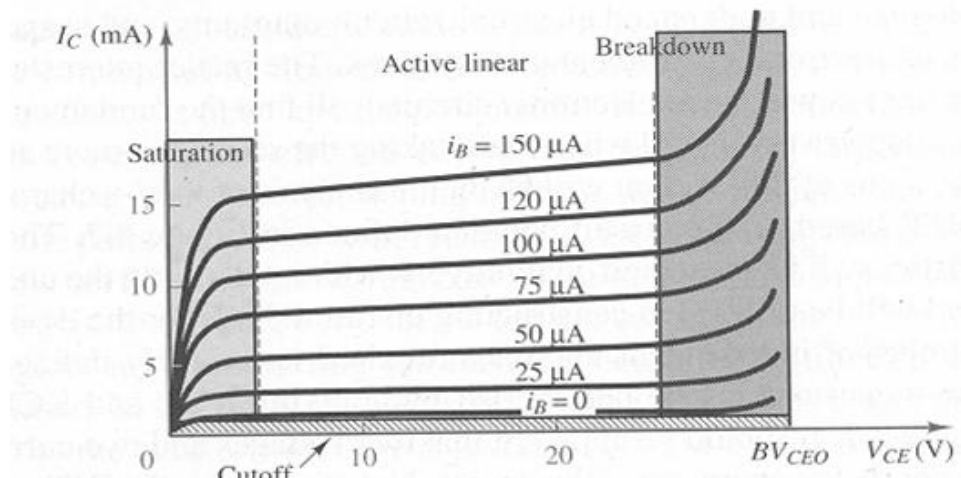
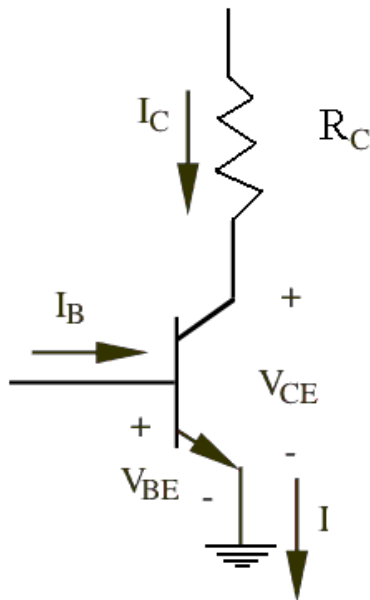


Figure 8.9(b) The collector-emitter output characteristics of a BJT

Common Emitter characteristics

Collector current controlled by the collector circuit.
([Switch behavior](#))

In full saturation
 $V_{CE} = 0.2V$.

Collector current proportional to Base current

The avalanche multiplication of current through collector junction occurs: to be avoided


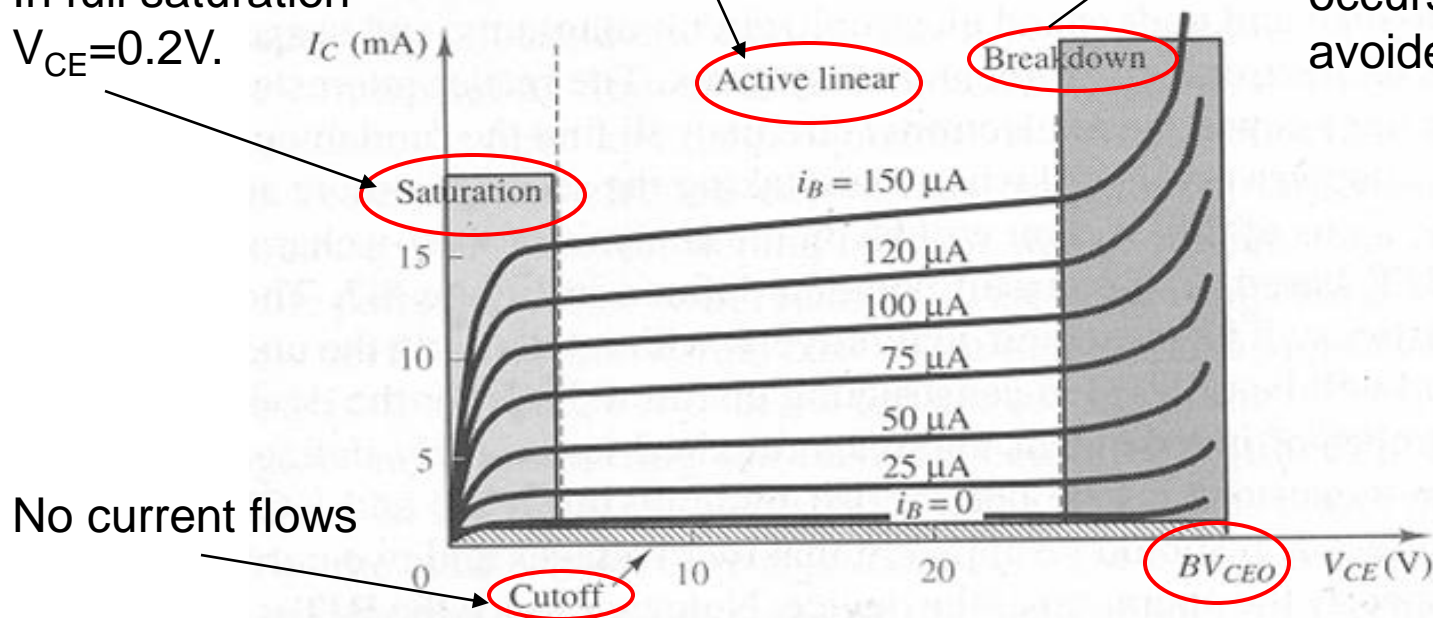


Figure 8.9(b) The collector-emitter output characteristics of a BJT

Operation region summary


Operation Region	I_B or V_{CE} Char.	BC and BE Junctions	Mode
Cutoff	$I_B =$ Very small	Reverse & Reverse	Open Switch
Saturation	$V_{CE} =$ Small	Forward & Forward	Closed Switch
Active Linear	$V_{CE} =$ Moderate	Reverse & Forward	Linear Amplifier
Break-down	$V_{CE} =$ Large	Beyond Limits	Overload

BJT as Switch

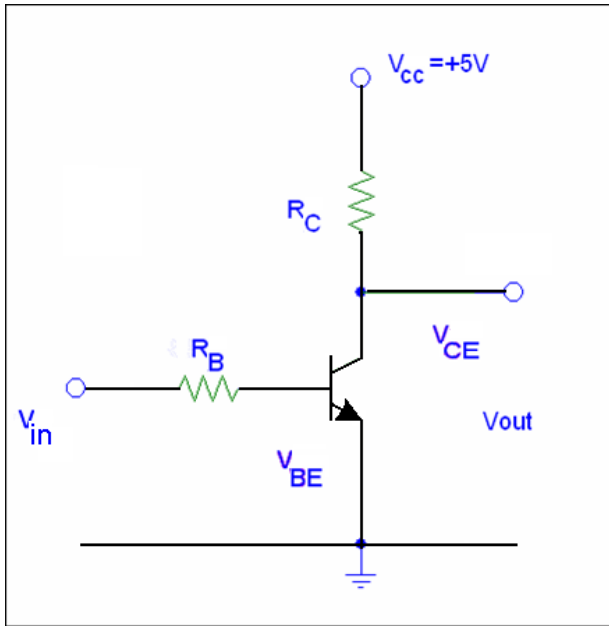

- $\underline{V_{in}}$ (Low) $< 0.7\text{ V}$
 - BE junction not forward biased
 - Cutoff region
 - No current flows
 - $V_{out} = V_{CE} = V_{CC}$
- $\underline{V_{out}} = \text{High}$

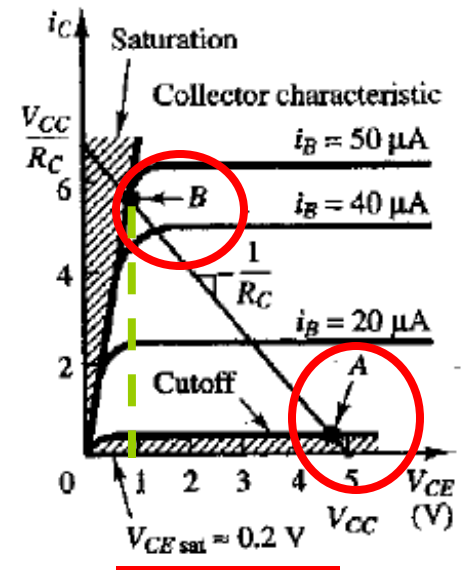
- $\underline{V_{in}}$ (High)
 - BE junction forward biased ($V_{BE} = 0.7\text{ V}$)
 - Saturation region
 - V_{CE} small ($\sim 0.2\text{ V}$ for saturated BJT)
 - $V_{out} = \text{small}$
 - $I_B = (V_{in} - V_B) / R_B$
- $\underline{V_{out}} = \text{LOW}$



BJT as Switch 2

- Basis of digital logic circuits
- Input to transistor gate can be analog or digital
- Building blocks for TTL – Transistor Transistor Logic
- Guidelines for designing a transistor switch:
 - $V_C > V_B > V_E$
 - $V_{BE} = 0.7 \text{ V}$
 - I_C independent from I_B (in saturation).
 - Min. I_B estimated from by ($I_{Bmin} \approx I_C/\beta$).
 - Input resistance \rightarrow such that $I_B > 5\text{-}10$ times I_{Bmin} because β varies among components, with temperature and voltage and R_B may change when current flows.
 - Calculate the max I_C and I_B not to overcome device specifications.

BJT as Amplifier

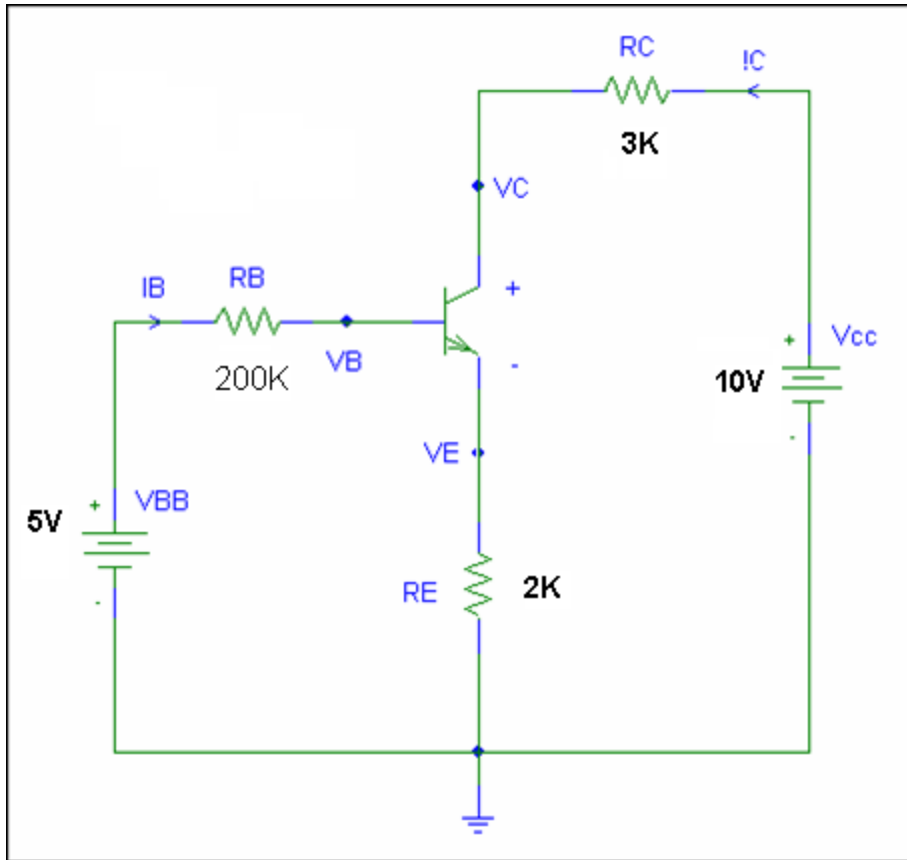


- Common emitter mode
- Linear Active Region
- Significant current Gain

Example:

- Let Gain, $\beta = 100$
- Assume to be in active region $\rightarrow V_{BE} = 0.7V$
- Find if it's in active region

BJT as Amplifier

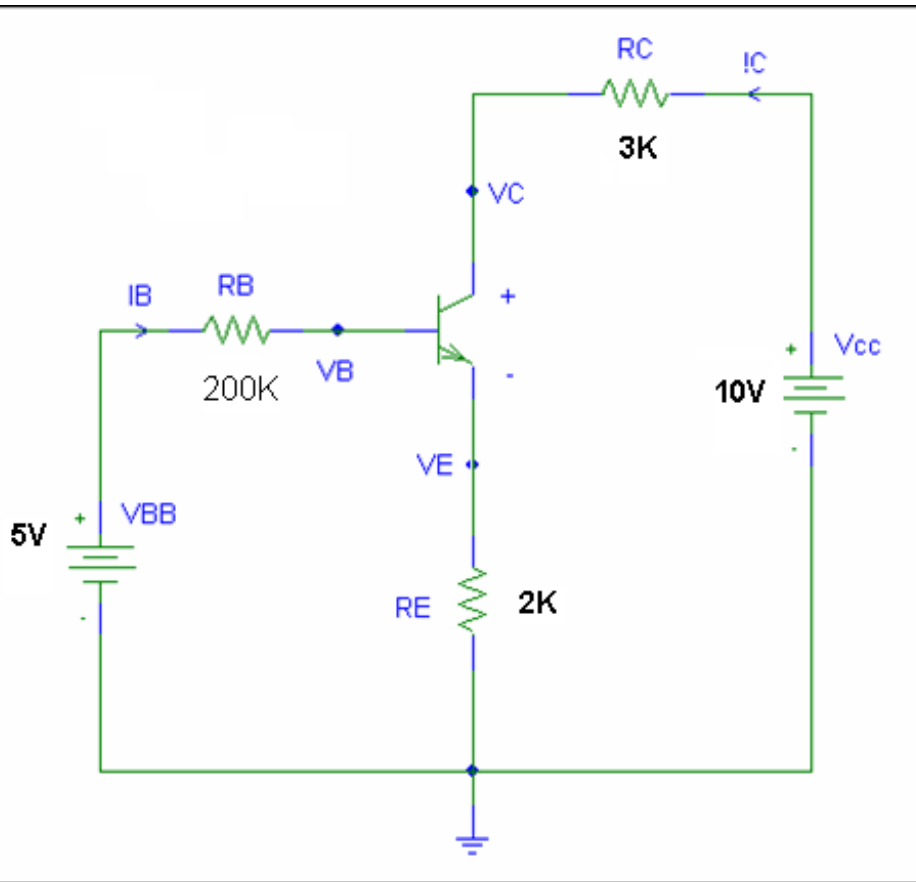

$$\underline{V_{BE}} = 0.7V$$

$$\underline{I_E} = I_B + I_C = (\beta + 1)I_B$$

$$\underline{I_B} = \frac{V_{BB} - V_{BE}}{R_B + R_E * 101} = \frac{5 - 0.7}{402} = 0.0107mA$$

$$\underline{I_C} = \beta * I_B = 100 * 0.0107 = 1.07mA$$

$$\begin{aligned} \underline{V_{CB}} &= V_{CC} - I_C * R_C - I_E * R_E - V_{BE} = \\ &= 10 - (3)(1.07) - (2)(101 * 0.0107) - 0.7 = \\ &= 3.93V \end{aligned}$$

$V_{CB} > 0$ so the BJT is in active region

Field Effect Transistors

- In 1925, the fundamental principle of FET transistors was established by Lilienfeld.
- 1955 : the first Field effect transistor works
- Increasingly important in mechatronics.
- Similar to the BJT:
 - Three terminals,
 - Control the output current


BJT Terminal	FET Terminal
Base	Gate
Collector	Drain
Emitter	Source

Field Effect Transistors


- Three Types of Field Effect Transistors
 - MOSFET (metal-oxide-semiconductor field-effect transistors)
 - JFET (Junction Field-effect transistors)
 - MESFET (metal-semiconductor field-effect transistors)
- Two Modes of FETs
 - Enhancement mode
 - Depletion mode
- The more used one is the n-channel enhancement mode MOSFET, also called NMOS

FET Architecture


Enhanced MOSFET

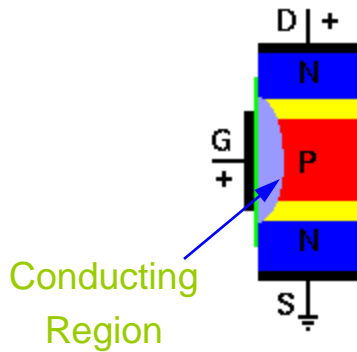

JFET

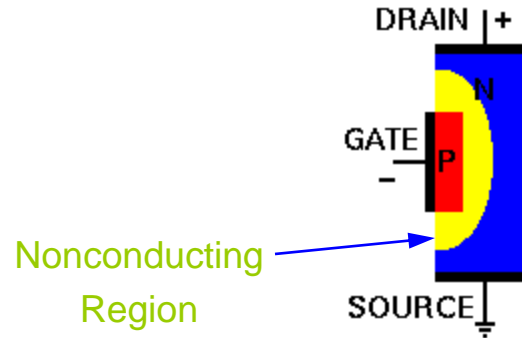

Depleted MOSFET

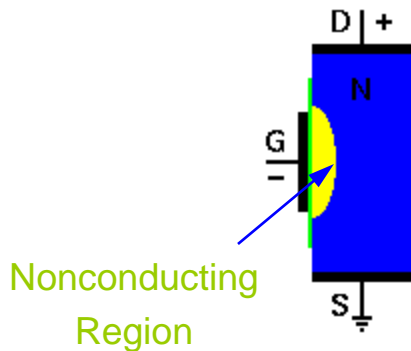

NMOS Voltage Characteristic

$$V_{GS} < V_{th}$$

$$I_{DS} = 0$$

$$V_{GS} > V_{th} :$$

$$0 < V_{DS} < V_{Pinch\ off}$$

Active Region

I_{DS} controlled by V_{GS}



$$V_{DS} > V_{Pinch\ off}$$

Saturation Region

I_{DS} constant

$$V_{DS} > V_{Breakdown}$$

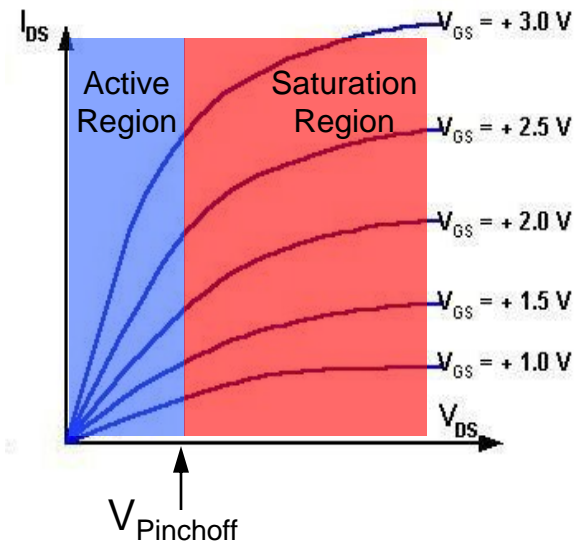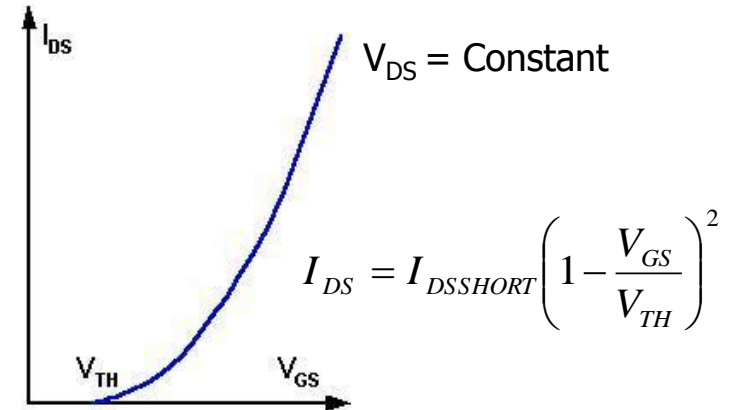I_{DS} approaches $I_{DSShort}$
Should be avoided



NMOS uses


- High-current voltage-controlled switches
- Analog switches
- Drive DC and stepper motor
- Current sources
- Chips and Microprocessors

- CMOS: Complementary fabrication


JFET overview



The circuit symbols:

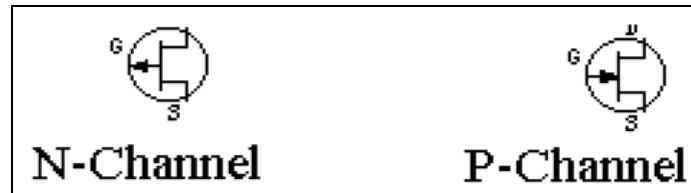

JFET design:

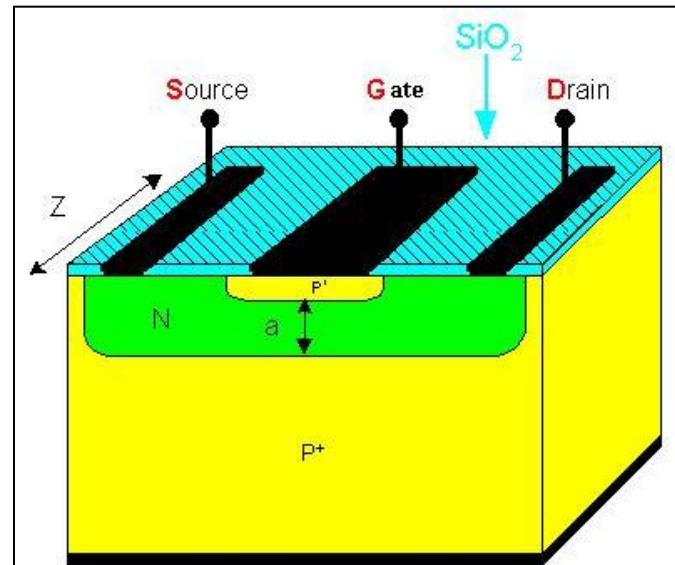


Junction Field Effect Transistor


$-V_{GS} > V_{th}$ Difference from NMOS
 $I_{DS}=0$
 $V_{GS} < -V_{th}$
 $0 < V_{DS} < V_{Pinch\ off}$
 Active Region
 I_{DS} controlled by

V_{GS}
 $V_{DS} > V_{Pinch\ off}$
 Saturation Region
 I_{DS} constant

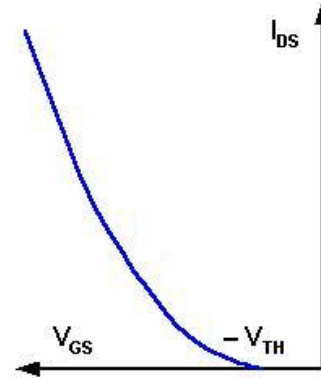
$V_{DS} > V_{Breakdown}$
 I_{DS} approaches
 $I_{DSShort}$
 Should be avoided


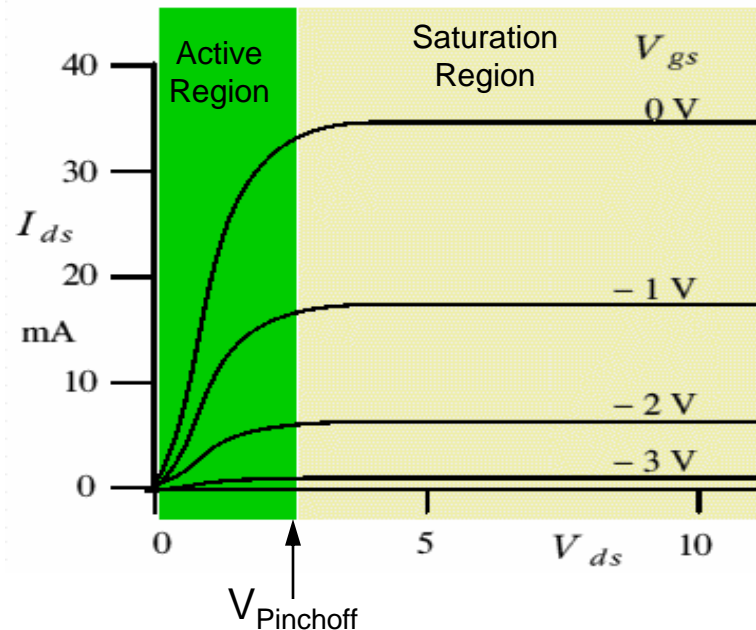
$$I_{DS} = I_{DSSHORT} \left(1 - \frac{V_{GS}}{V_{TH}} \right)^2$$




JFET uses

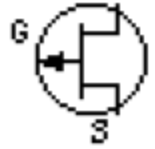

- Small Signal Amplifier
- Voltage Controlled Resistor
- Switch

FET Summary

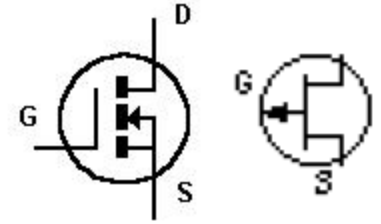

- General:
 - Signal Amplifiers
 - Switches

JFET:

For Small signals

Low noise signals

Behind a high impedance system

Inside a good Op-Ampl.

MOSFET:

Quick



Voltage Controlled Resistors

RDS can be really low : 10 mOhms

Power Transistors

- In General
 - Fabrication is different in order to:
 - Dissipate more heat
 - Avoid breakdown
 - So Lower gain than signal transistors
- BJT
 - essentially the same as a signal level BJT
 - Power BJT cannot be driven directly by HC11
- MOSFET
 - base (flyback) diode
 - Large current requirements

Other Types of Transistors

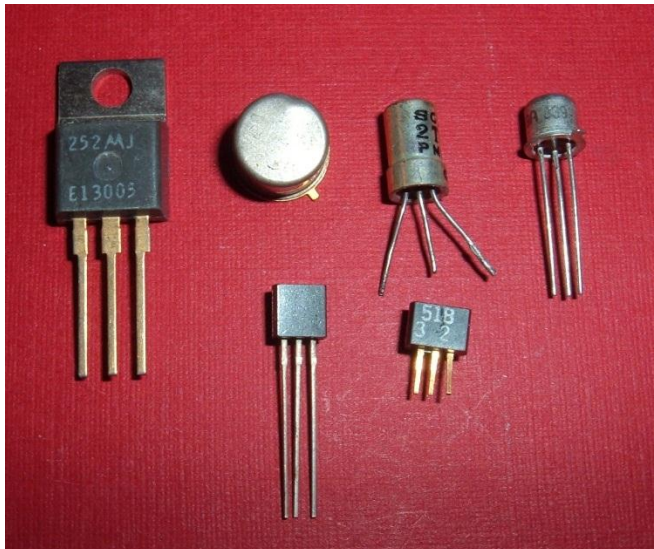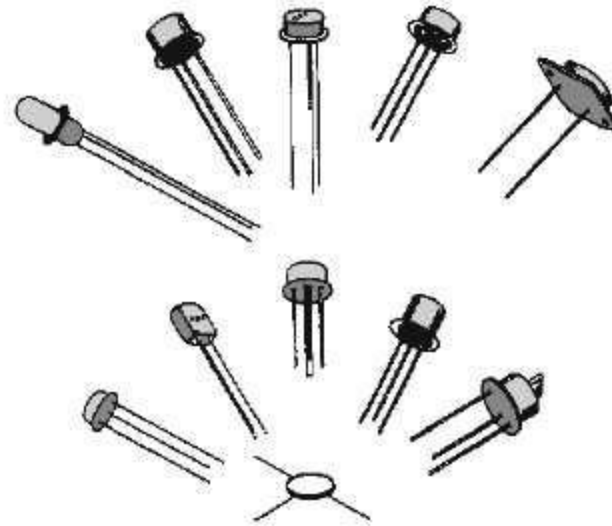


Typical transistor packages

Various Types of Transistors

- TempFET – MOSFET's with temperature sensor
- High Electron Mobility Transistors (HEMTs) – allows high gain at very high frequencies
- Darlington – two transistors within the same device, gain is the product of the two individual transistors

Shockley Diode/Thyristor

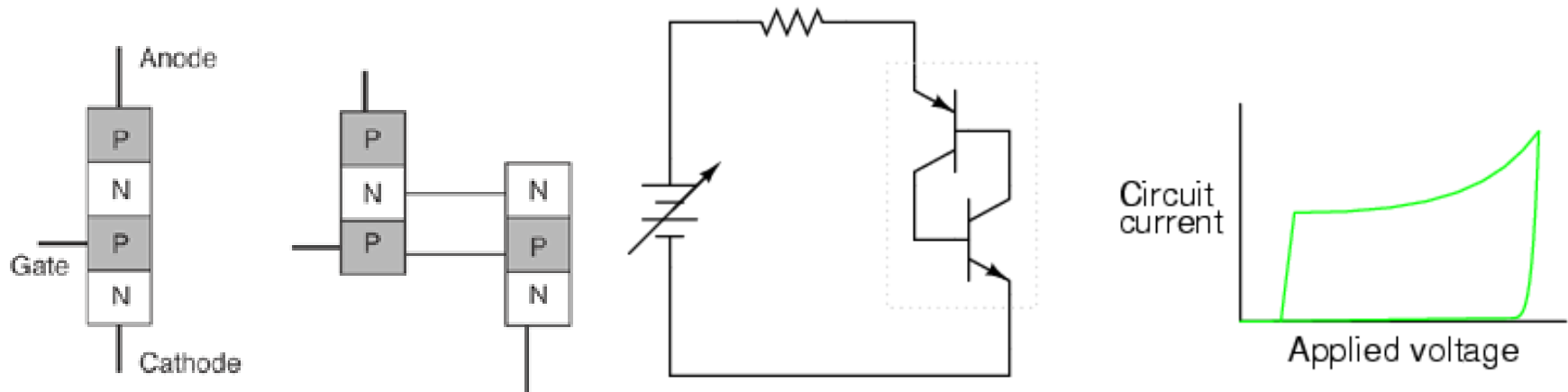- Four-layer PNPN semiconductor devices
- Behaves as two transistors in series
- Once on, tends to stay on
- Once off, tends to stay off



TRIAC

- Triode alternating current switch
- Essentially a bidirectional thyristor
- Used in AC applications
- Con: Requires high current to turn on
- Example uses: Modern dimmer switch

