

# **Analog Sensors**

# 6.3 Analog Sensors

- ⌘ A number of sensors have analog output signal rather than digital signals
- ⌘ A/D converter is required to connect to CPU
- ⌘ Examples:
  - Microphone
  - analog infrared distance sensor
  - analog compass
  - barometer sensor

# Ohm's Law

⌘ **Ohm's law;** explains the relationship between voltage (V), current (I), and resistance (R):

$$V = I R$$

⌘ **Simply put:** the voltage between two points in an electronic circuit is equal to the product of the amount of current flowing through them and the amount of resistance between them.

⌘ Voltage is measured in **Volts** (V), current in **Amperes** (A), and resistance in **Ohms** (Omega).

# Combining resistances

- ⌘ It's not hard to figure out how much resistance one resistor gives (since they are labeled!).
  - ⊞ But what happens if you put one resistor  $R_1$  after another  $R_2$ , i.e., connected them *in series*?
- ⌘ The current  $I$  flowing through any number of resistors has to be equal, since it has only one route to flow on, as it goes from one resistor to the next.
  - ⊞ What happens to the voltage  $V$ ?
- ⌘ Recall Ohm's law:  $V = I R$ 
  - ⊞  $V = I (R_1 + R_2)$
  - ⊞  $V = I R_1 + I R_2$
- ⌘ Suppose we measure the voltage across  $R_1$ , i.e., the voltage between the input point  $V$  and the connection between  $R_1$  and  $R_2$ , would would it be?
  - ⊞ It would be  $I R_1$  Volts. Similarly, if we measure the voltage across  $R_2$ , i.e., the voltage between the connection between  $R_1$  and  $R_2$  and ground, what will it be? It will be  $I R_2$ .
- ⌘ The total voltage in an electronic circuit has to add up; therefore, the input voltage  $V$  has to equal the output voltage, after the drop across the two resistors,  $R_1$  and  $R_2$ .
- ⌘ Therefore, since voltages in a series add, so do resistances in a series.

Practical use of your  
undergraduate electronics

# Dividing voltage

- ⌘ Suppose we take the voltage out at the point between R1 and R2, what will the amount of that voltage  $V_{out}$  be?
- ⌘ Use Ohm's law again:  $V = I R \Rightarrow I = V / R$   
$$= V / (R1 + R2)$$
- ⌘ Then the voltage drop across R2, is the product of the above current I and R2:  
$$\boxed{V_{out} = V R2 / (R1 + R2)}$$
- ⌘ What if  $R1 = R2$ ?  
$$= V R2 / 2 R2$$
  
$$= V / 2$$
- ⌘ This is a **voltage divider**. To summarize: voltage can be divided by using two equal-value resistors in series.
- ⌘ You will learn in the lab how to bridge the gap between this type of laws of electronics to physical sensors all the way to robot behavior.


# Analog Sensors

- ⌘ The analog ports all have a **pull up resistor** which is a 47K resistor between +5 volts and the signal input.
- ⌘ The analog readings are generated by **measuring the amount of current flow** through the pull up resistor.
- ⌘ If no current flows through the resistor, the voltage at the signal input will be +5 volts and the **analog value will be 255**.


- The voltage at the signal pin can be simply calculated by:

$$V_{sig} = 5$$

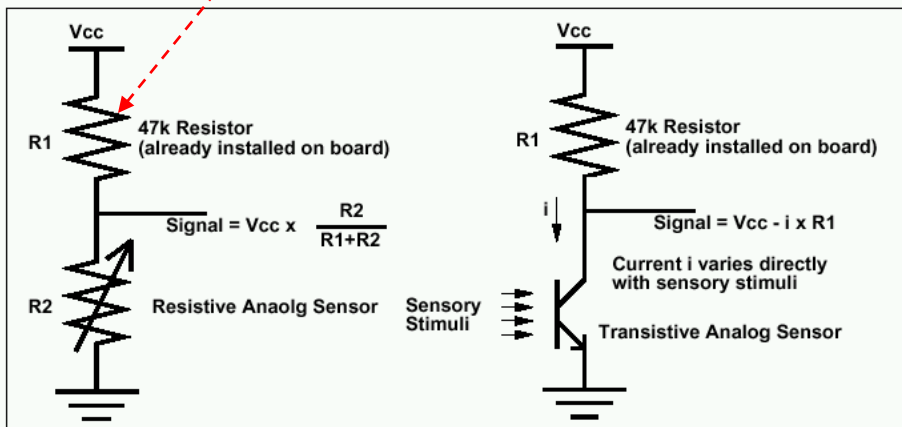- check if one sensor fell out: write a piece of code that checks the values of the analog ports that you have sensors plugged into.
- If that value is above 250 or so, have it tell you to check the sensor.



# Figure 5.4: Analog Sensors Schematics

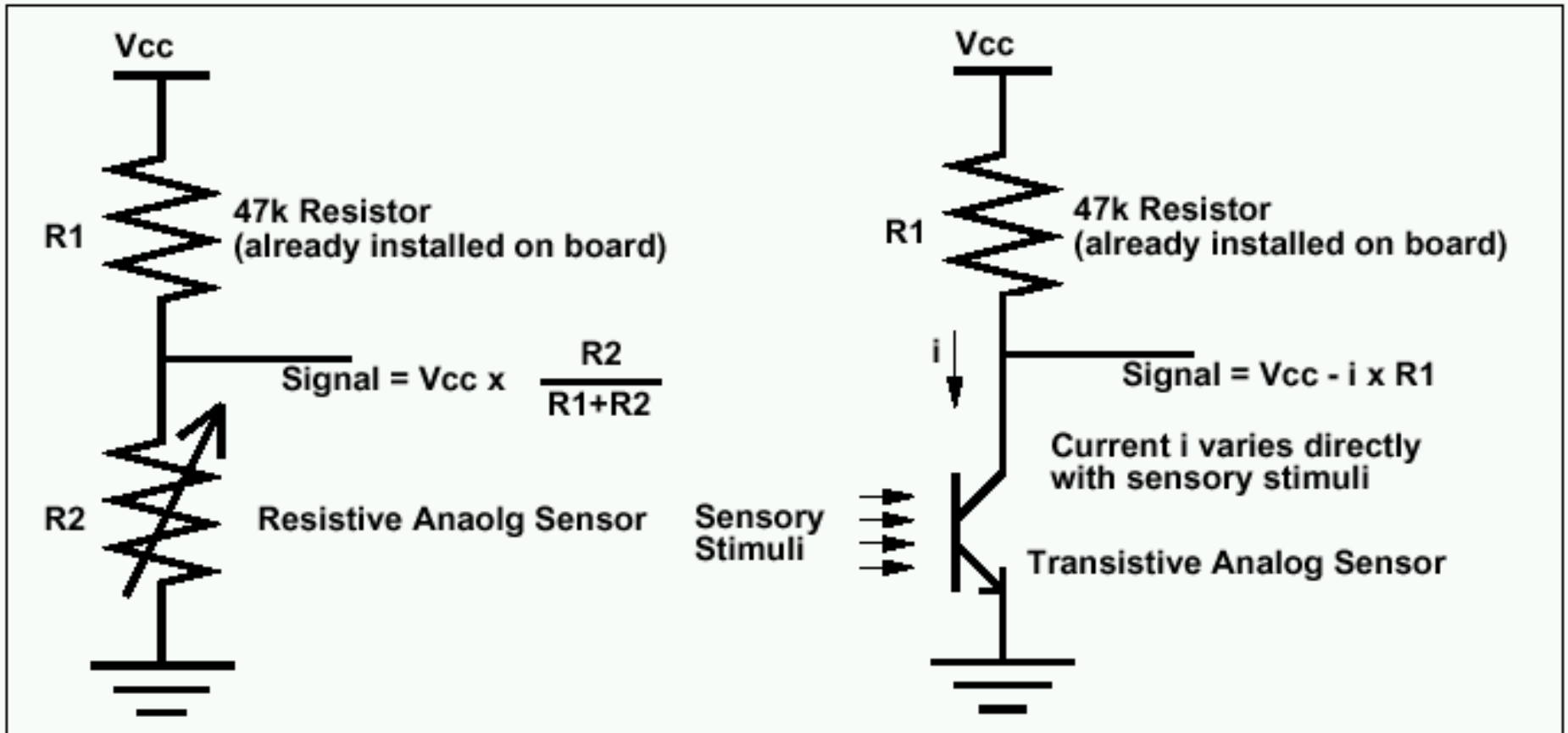


# Resistive Sensors

⌘ The resistance of resistive analog sensors, like the bend sensors or potentiometers, change with changes in the environment:

- ☒ an increase in light,
- ☒ or a physical deformation.

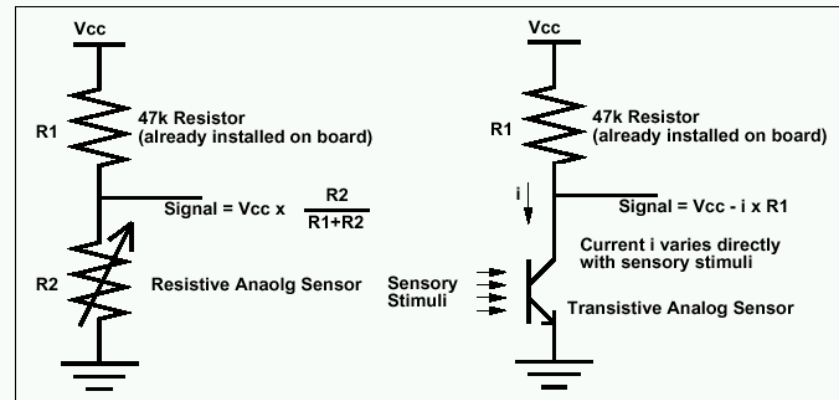⌘ The change in resistance causes a change in the voltage at the signal input by the voltage divider relation.



$$V_{sig} = \frac{R_{sensor}}{47\Omega + R_{sensor}} * 5V$$



# Transitive Analog Sensor

- ⌘ Transitive analog sensors, like the **photo transistors** and **reflectance sensors**, work like a **water faucet**.
- ⌘ Providing more of what the sensor is looking for **opens the setting of the valve**, allowing more current to flow.
- ⌘ This makes the voltage at the signal decrease.
- ⌘ A **photo transistor** reads around **10 in bright light** and **240 in the dark**.
- ⌘ One problem that may occur with transitive sensors is that the voltage drop across the resistor may not be large enough when the transistor is open.
  - ⊠ Some transitive devices only allow a **small amount of current** to flow through the transistor.

# Transitive Analog Sensor (cont)

- ⌘ A larger range for the sensor can be accomplished by putting a **larger pull-up resistor**.
  - ☒ By having a larger resistor, the voltage drop across the pull-up resistor will be proportional to the resistance.
- ⌘ Martin's book gives examples of use and mountings **for each type of sensor**.
- ⌘ Keep in mind that these are only simple examples and are not the only possible uses for them.
- ⌘ It's **up to you** to make creative use of the sensors you have.

# Sensor Interfacing to Analog Inputs


•  $V_{\text{sens}}$  voltage at the center tap of the two resistors is proportional to the ratio of the two resistances.

$$R_{\text{photo}} = 47\text{K}\Omega, V_{\text{sens}} = 2.5 \text{ v (exactly)}$$

$$R_{\text{photo}} \ll 47\text{K}\Omega, V_{\text{sens}} \approx \text{gnd}$$

$$R_{\text{photo}} \gg 47\text{K}\Omega, V_{\text{sens}} \approx +5 \text{ v}$$

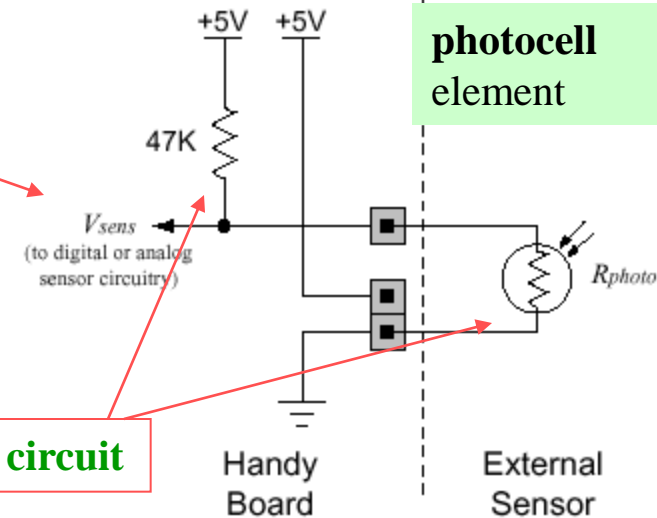Two resistors form **voltage divider circuit**




Also possible to connect circuits that generate a voltage
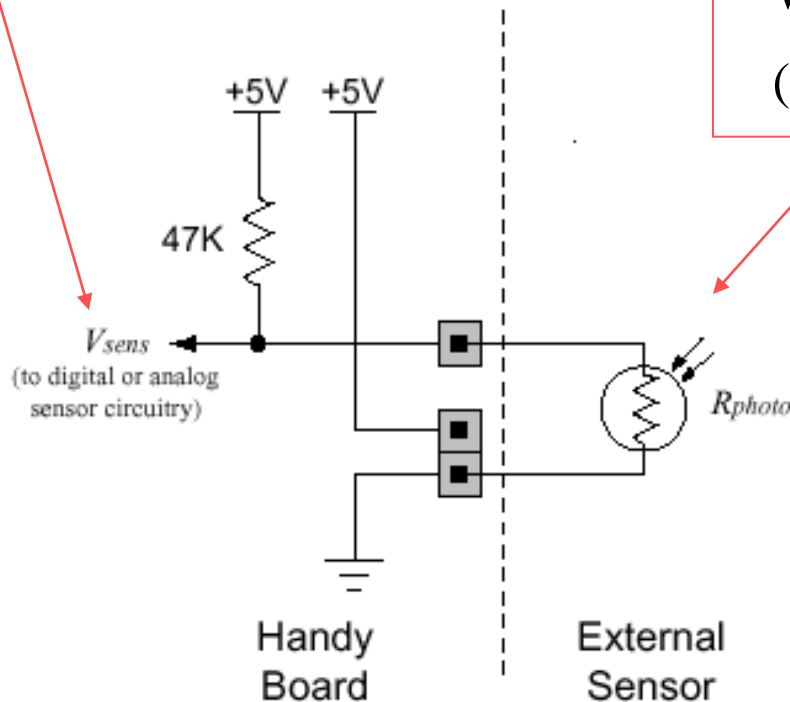
# Sensor Interfacing to Analog Inputs

0 to 5 volts are converted into 8-bit numbers 0 to 255 (decimal)  
**(A/D conversion)**

- When the photocell resistance is small (brightly illuminated), the  $V_{sens} \approx 0v$
- When the photocell resistance is large (dark),  $V_{sens} \approx +5v$



# Resistive Position Sensors


Potentiometers. Glows. Pads. Bend  
Sensors. Other....?
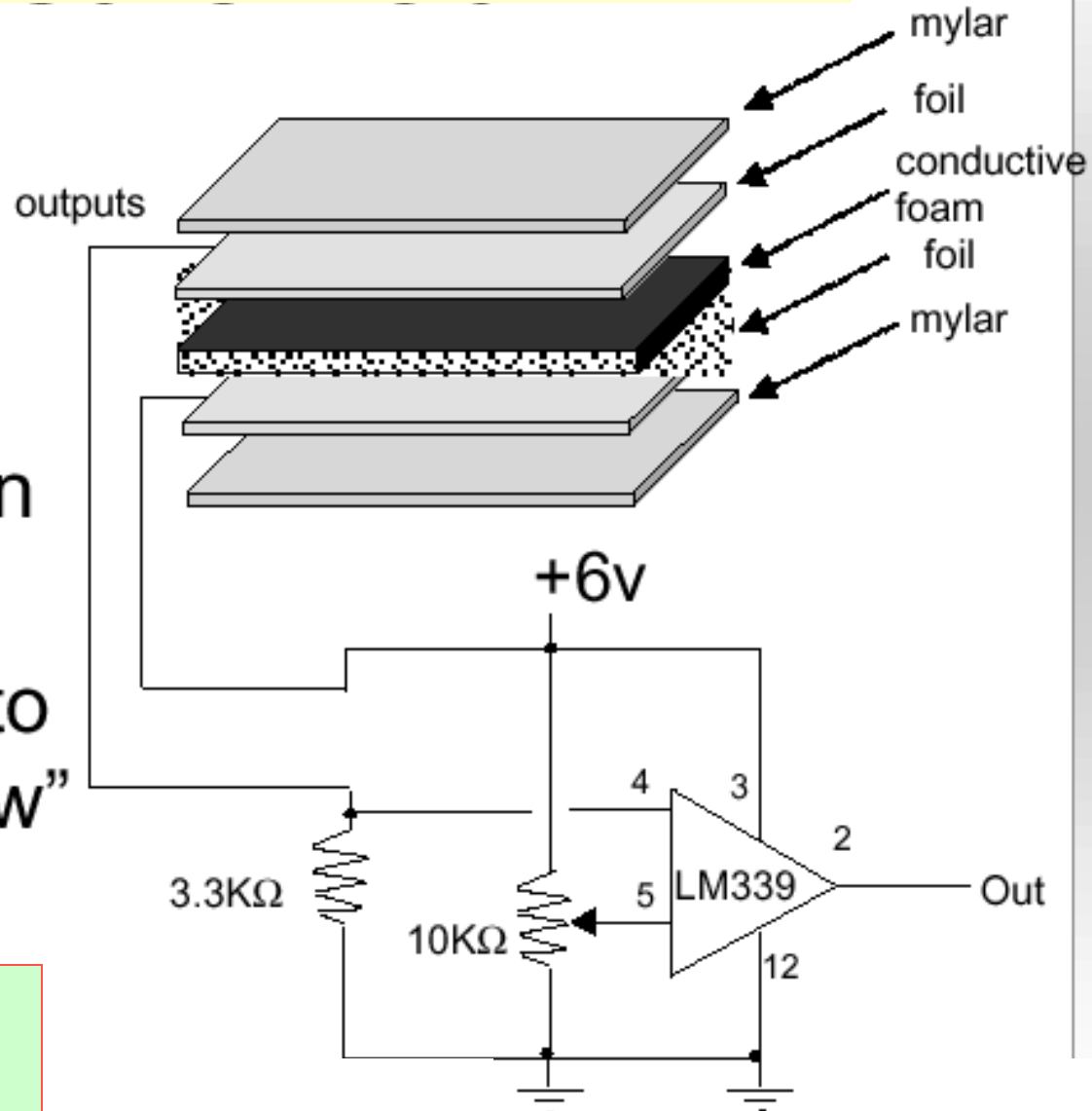
# Pressure Pad



- Often used in grippers to detect the amount of pressure applied in picking up objects
- Relatively simple to build a “home-brew” version

You can purchase such pad for Nintendo games




# Pressure Pad


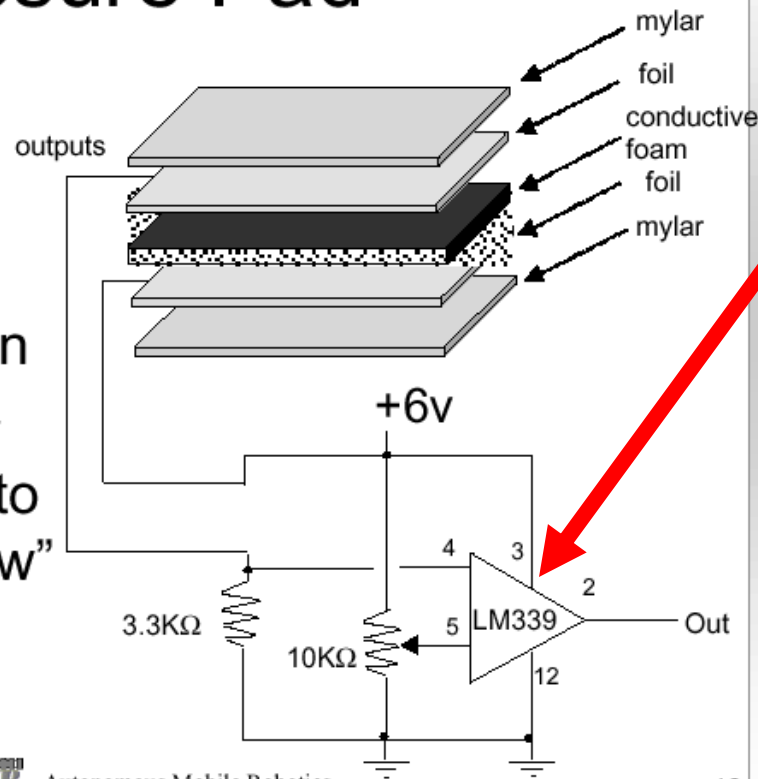
## Pressure Pad

- Often used in grippers to detect the amount of pressure applied in picking up objects
- Relatively simple to build a “home-brew” version



⌘ LM339 is a **quad comparator circuit**:

⊠ Output will be +6V

⌘ Another approach is to use **ohm meter** to detect the resistance change which would be proportional to **amount of pressure applied**.


# Potentiometer: the main ideas

- ⌘ **Potentiometers** are very common for manual tuning; you know them from some controls (such as volume and tone on stereos).
- ⌘ Typically called *pots*, they allow the user to manually adjust the resistance.
- ⌘ The general idea is that the device consists of a movable tap along two fixed ends.
- ⌘ As the tap is moved, the resistance changes.
- ⌘ As you can imagine, the resistance between the two ends is fixed, but the resistance between the movable part and either end varies as the part is moved.
- ⌘ In robotics, pots are commonly used to *sense* and **tune position** for sliding and rotating mechanisms.


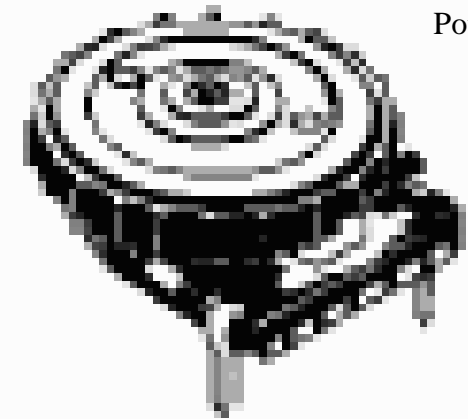
# Potentiometers versus resistance sensors


- Fixed Rotation Sensors
- Easy to find, easy to mount



Potentiometer
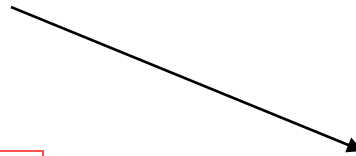
## Light Sensor

- Good for detecting direction/presence of light
- **Non-linear** resistance
- Slow response



Cadmium Sulfide Cell

Look to catalogs:

**HANDYBOARD:** Gleason Research. <http://www.gleasonresearch.com/>

<http://handyboard.com>

**DISTRIBUTOR OF AGE BEND SENSOR:** Images Company:

<http://www.imagesco.com>

**PITSCO LEGO DACTA, JAMECO, ETC** - see the book and my webpage.

# Potentiometers

- Manually-controlled variable resistor, commonly used as volume/tone controls of stereos

- **Mechanical varieties:**




- **Linear** and **rotational** styles - make position sensors for both sliding mechanisms and rotating shafts

- Resistance between the **end taps** is fixed, but the resistance between either end tap and the **center swipe** varies based on the position of the swipe




- **Electrical varieties:**

- **Linear taper** - linear relationship between position and resistance. Turn the pot 1/4 way, the resistance between the nearer end and the center is 1/4 of end-to-end resistance

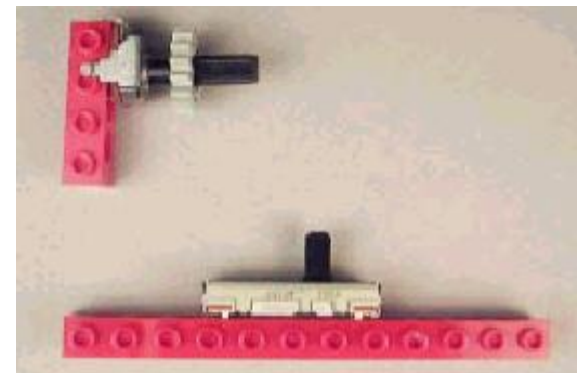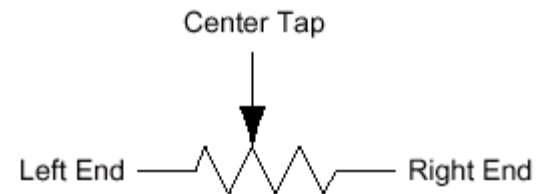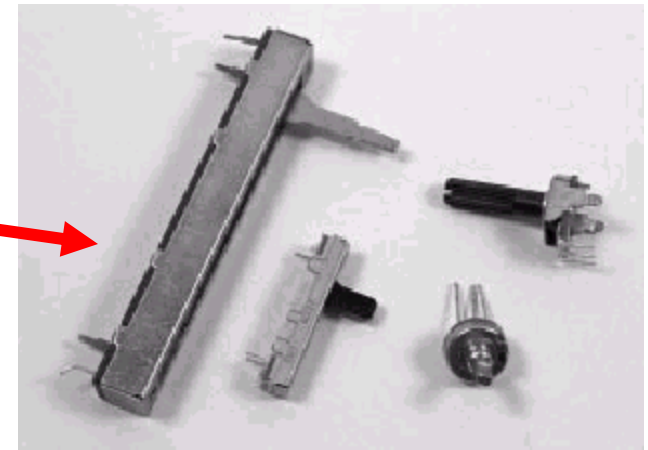- **Audio taper** - *logarithmic* relationship between position and resistance. At one end, 1/4 turn would swipe over a small bit of total resistance range, while at the other end, 1/4 turn would be most of the range





# Figure 5.5: Potentiometer Assemblies

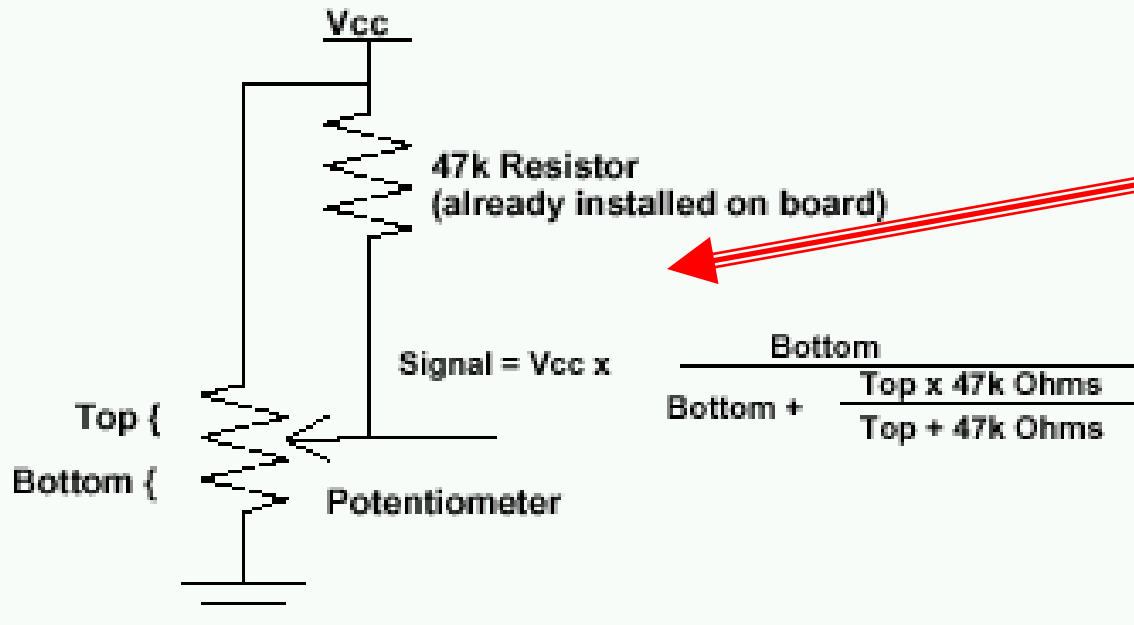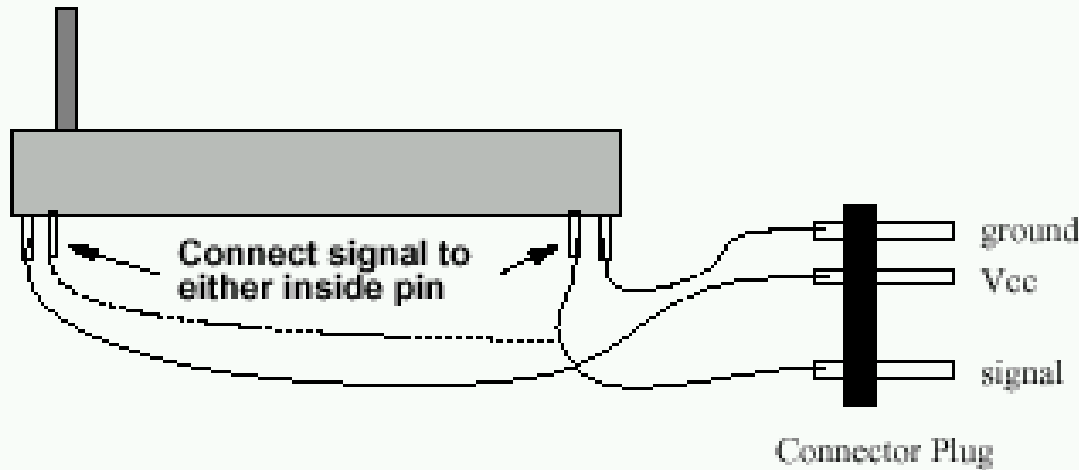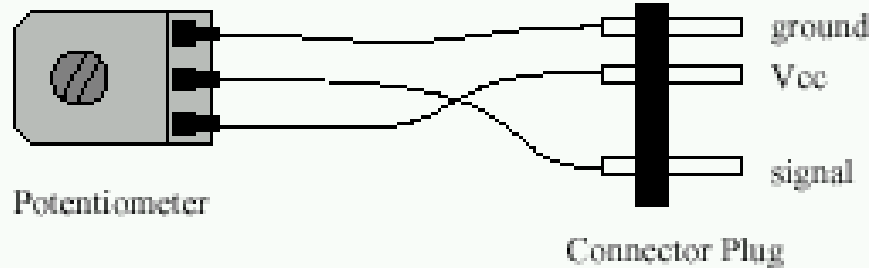

- ⌘ Kits contain several sizes of potentiometers, also known as variable resistors.
- ⌘ Potentiometers should be wired with Vcc and ground on the two outside pins, and the signal wire on the center tap.
  - ⊠ This will, in effect, place the resistance of the potentiometer in parallel with the 47K pull-up on the expansion board and is **more stable** than just using one side and the center tap to make a plain variable resistor
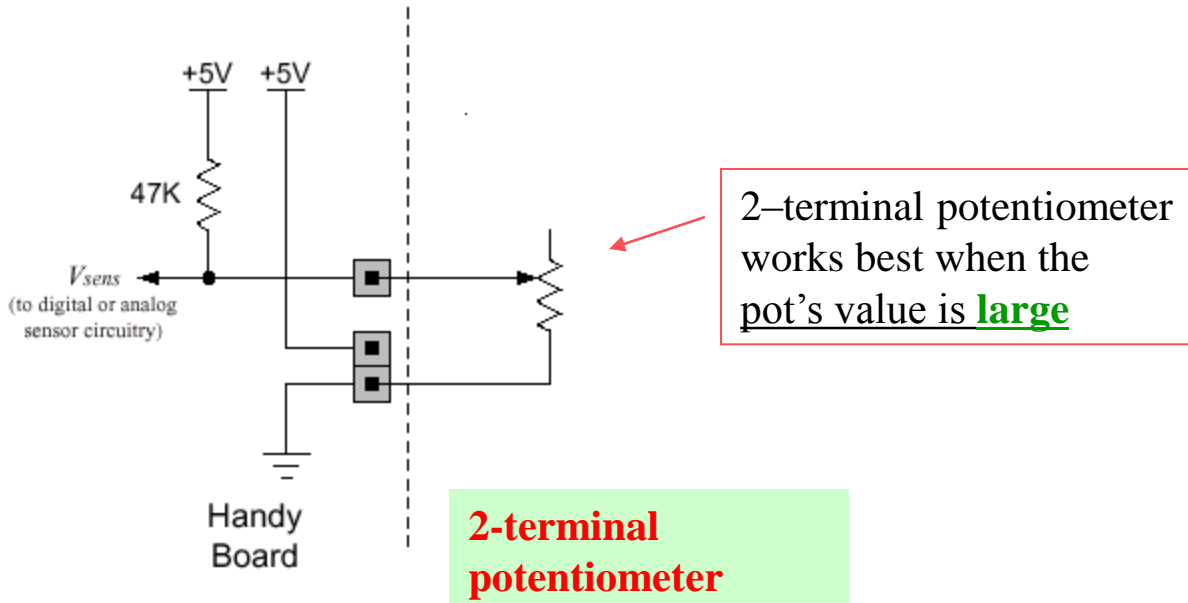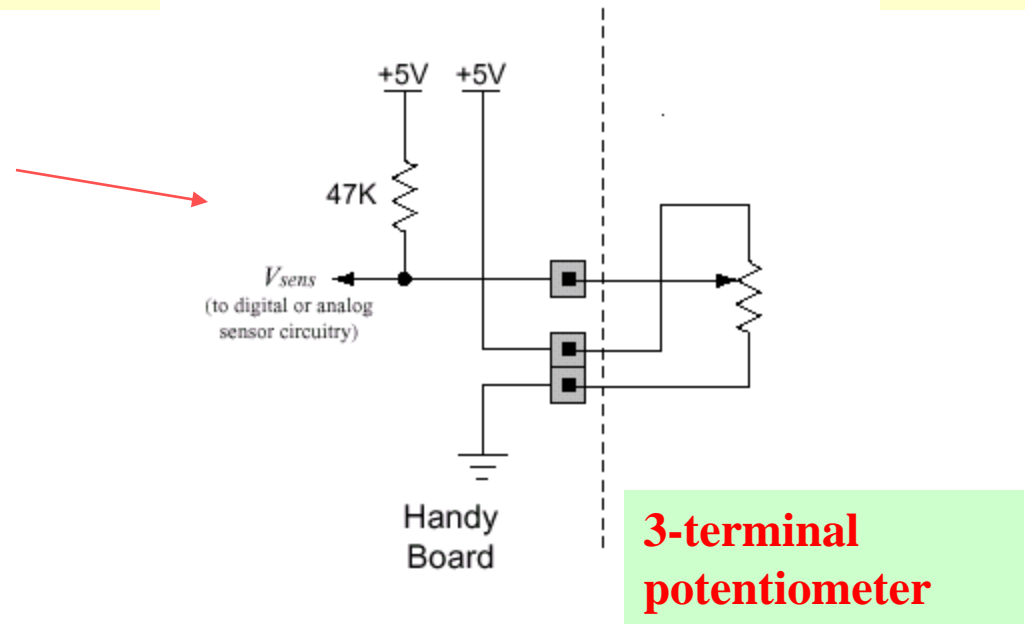
# Two ways of using Potentiometers as Resistive Position Sensors

works best when the potentiometer resistance is small enough such that a 47K resistance in parallel with the pot's resistance has only a small effect



2-terminal potentiometer works best when the pot's value is large

# Various uses of Potentiometers

- ⌘ Potentiometers have a **variety of uses**:
  - ☒ In the past, they have been used for **menuing programs**
  - ☒ For **angle measurement** for various **rotating limbs**
  - ☒ For scanning **beacons**.
- ⌘ They can be **used with a motor** to **mimic servos**, but that's a difficult task.
  - ☒ It is important to notice that the pots are *not designed to turn more than about 270 degrees.*
  - ☒ Forcing them farther is likely to break them.

Tell about our previous project of animation inverse kinematics robot with many pots and A/D board. (the one that was stolen)

# Various uses of Potentiometers

- ⌘ A potentiometer can be attached to a LEGO beam
  - ☒ such that it can be used in place of a bend sensor.
  - ☒ The rotation of the beam will produce a rotation in the potentiometer.
- ⌘ See if you can come up with an assembly that can be used in place of a bend sensor.
  - ☒ The advantage to such a sensor is that it is much sturdier than the bend sensor.
  - ☒ The disadvantage is that it is bulkier.

# Linear Potentiometers and their use in HandyBoard

- ⌘ A linear potentiometer can be used to measure precise linear motion,
  - ⊞ such as a [gate closing](#),
  - ⊞ or a [cocking mechanism](#) for ring balls or blocks.
- ⌘ **Frob-knob**
  - ⊞ The frob knob is the [small white dial](#) on the lower left corner of the Expansion Board.
- ⌘ *It returns values between 0 and 255* and provides a handy user input for adjusting parameters on the y or for menuing routines to select different programs.
- ⌘ You may find it useful to [glue a small LEGO](#) piece to the frob knob to make turning it easier.

# Homework Assignment

- ⌘ Try to find in your storage any kind of sensors that you do not use and bring them to the robotics labs.
- ⌘ The ECE 271 and the high school students will possibly use it for projects if you will not.
- ⌘ Look around the lab and try to identify sensors and devices that we talked about.




# **Resistive (Analog) Position Sensors**

# Resistive Position Sensors: bending

- ⌘ We said earlier that a **photocell** is a resistive device, i.e., it senses resistance in response to the light.
- ⌘ We can also sense resistance in response to other physical properties, such as ***bending***.
  - ⊞ **The resistance of the device increases with the amount it is bent.**
- ⌘ These **bend sensors** were originally developed for video game control
- ⌘ They are generally quite useful:
  - ⊞ Nintendo Powerglove
  - ⊞ **Video game accessories** are in general useful for robotics and virtual reality and very cheap.


# Resistive Bend Sensors

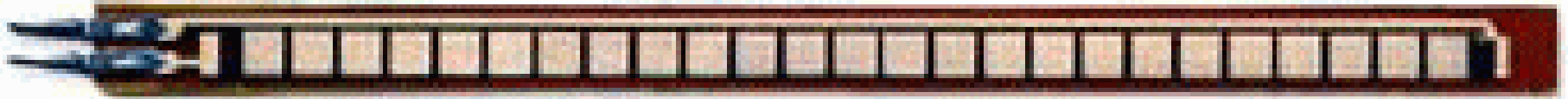

- Resistance = 10k to 35k
- Force to produce 90deg = 5 grams
- [www.jameco.com](http://www.jameco.com) = 10\$

# Bend Sensors

You can remove it  
from Nintendo gloves

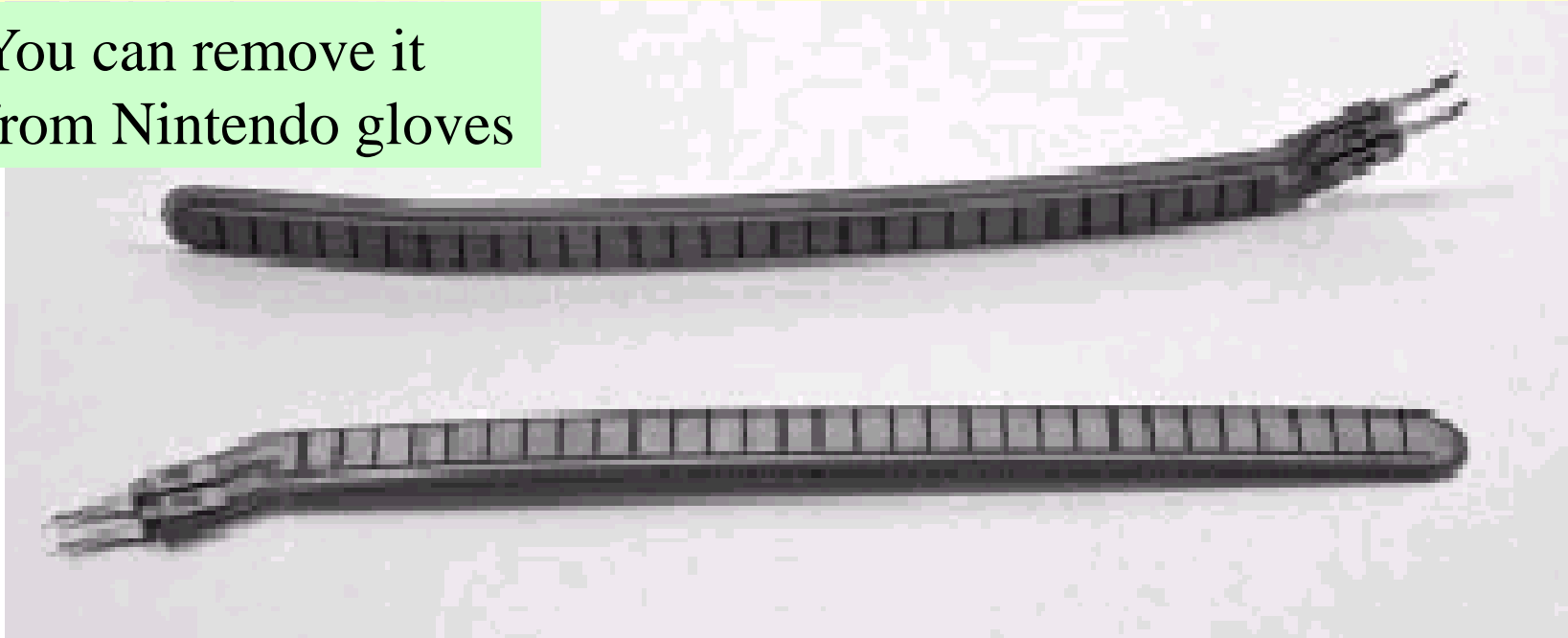


- Useful for **contact sensing** and **wall-tracking**
- The bend sensor is a simple resistance
  - As the **plastic strip is bent** (with the silver rectangles facing outward), the **resistance increases**

# Resistive Position Sensors


- ⌘ Mechanically, the bend sensor is **not terribly robust**, and requires strong protection at its base, near the electrical contacts.
  - ⊞ Unless the sensor is well-protected from direct forces, it will fail over time.
- ⌘ Notice that even in a good arrangement, repeated bending will **wear out** the sensor.
- ⌘ **Remember:** a bend sensor is much *less robust* than light sensors,
  - ⊞ although they use the same underlying **resistive principle**.

# Applications of Resistive Analog Sensors


⌘ Measure bend of a joint

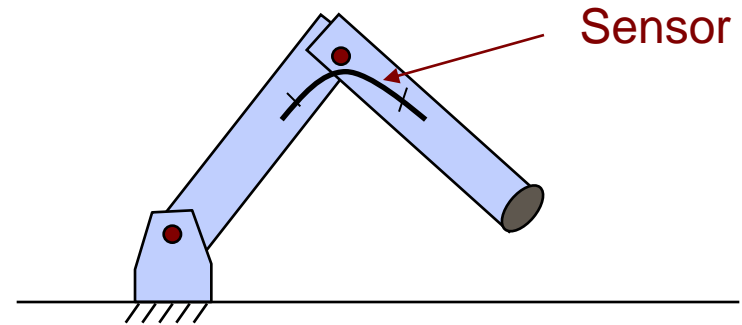

⌘ Wall Following/Collision Detection

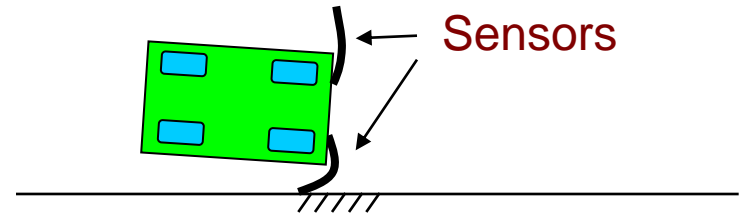

⌘ Weight Sensor

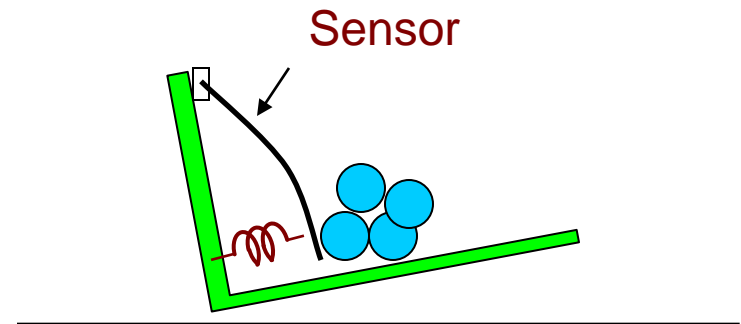


# Inputs for Resistive Sensors

Voltage divider:


You have two resistors, one is fixed and the other varies, as well as a constant voltage

$$V1 - V2 * (R2/R1+R2) = V$$


Known **unknown** **measure**

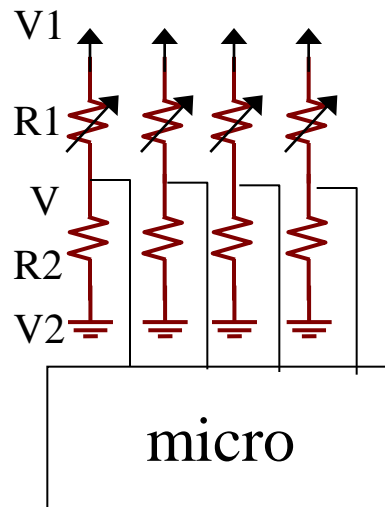

Analog to Digital  
(pull down)

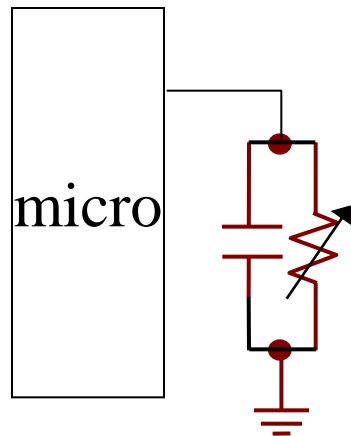

Single Pin  
Resistance  
Measurement

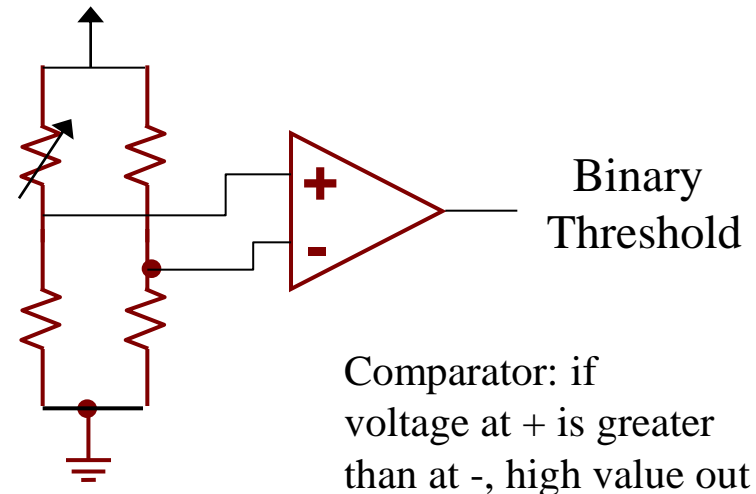

# Sensor Assembly

⌘ You should have read the section on the chapter of Martin's book on the types of connectors used with the 6.270 board.

☑ This is an important concept to understand before building your sensors.

⌘ When building your sensors, do not make your wires too long.

☑ Excess wiring has a tendency to get caught in gears and other mechanisms.




# Sensor Assembly Homework

- ⌘ Start out with sensor wires **no longer than 1 foot** long and when you finally decide on your robot configuration, you can modify to length.
  - ☒ Just build a few of each type so you can play with them.
- ⌘ Start out with building simple sensors like one or two **switches**.
- ⌘ The more complicated ones will be the analog sensors that use IR.
- ⌘ Go to lab and familiarize yourself with **Lego kit** sensors and how to use them.
- ⌘ I purchased many good sensors from Wacky Willy, Tek Country Store and Radio Shack. In Goodwill you can buy old toys like Nintendo gloves or jumping pads that can be used. They are in the lab and you can use them. You have to notify me or lab assistant.


# 6.4 A/D Converter

- Signal has to be provided at correct level, e.g. between 0 .. 5V
- If multiple channels are read: low internal resistance of signal line is important
- A/D converter translates analog voltage level into digital value
- Digital output from A/D converter can be
  - parallel  
(e.g. 8 bit, direct connection to data bus)
  - serially digital  
(provide programmed clock signal to converter to read data bit by bit)


# A/D Converter

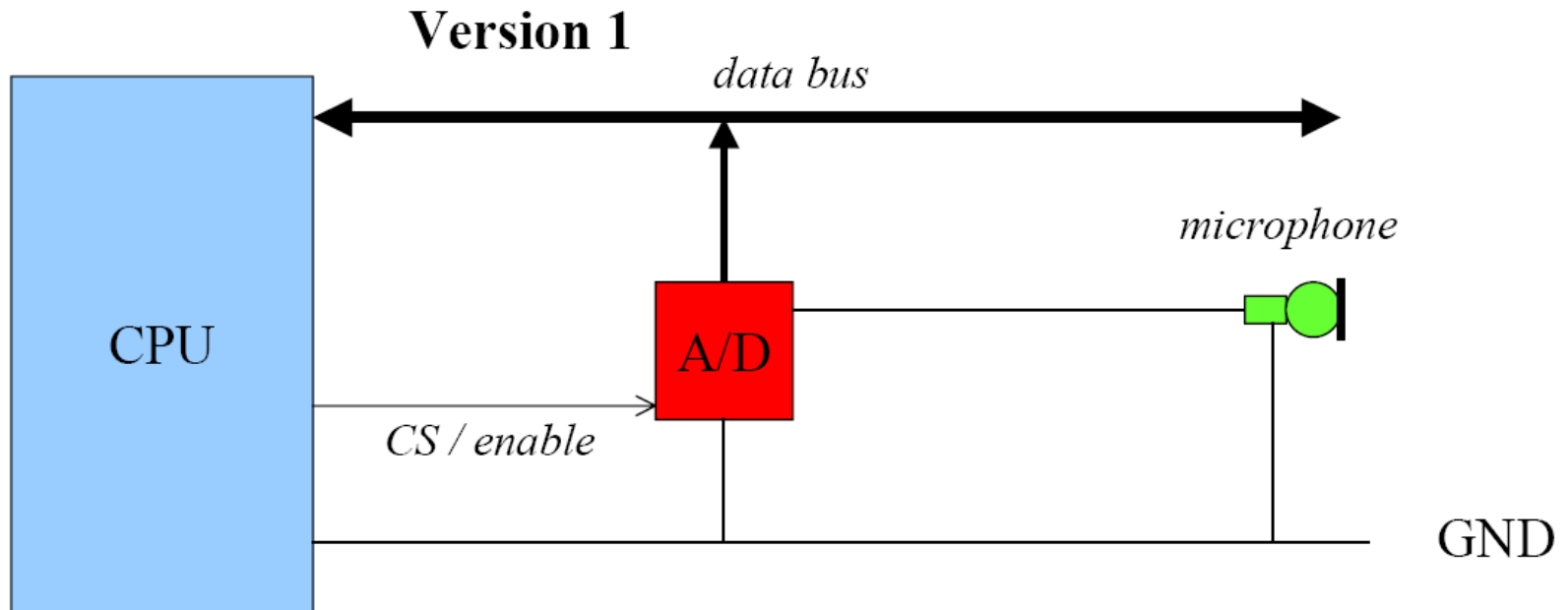

# A/D Converter

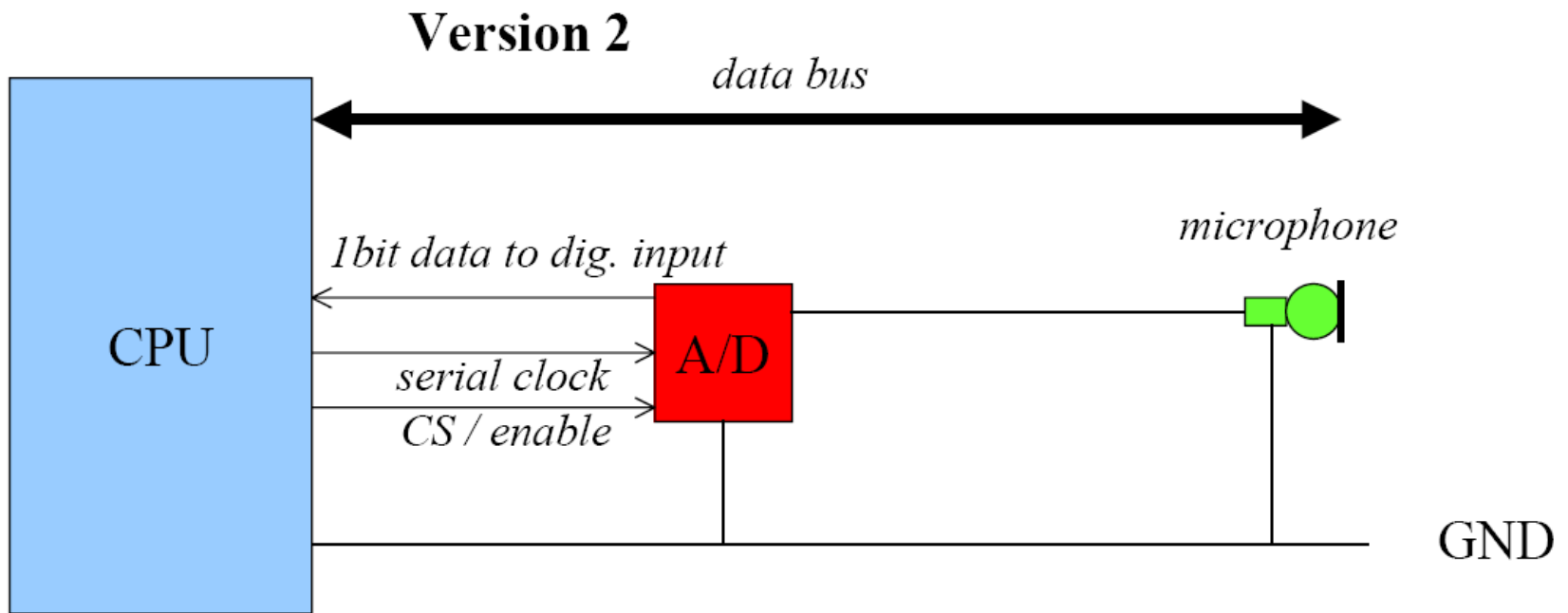

# A/D Converter

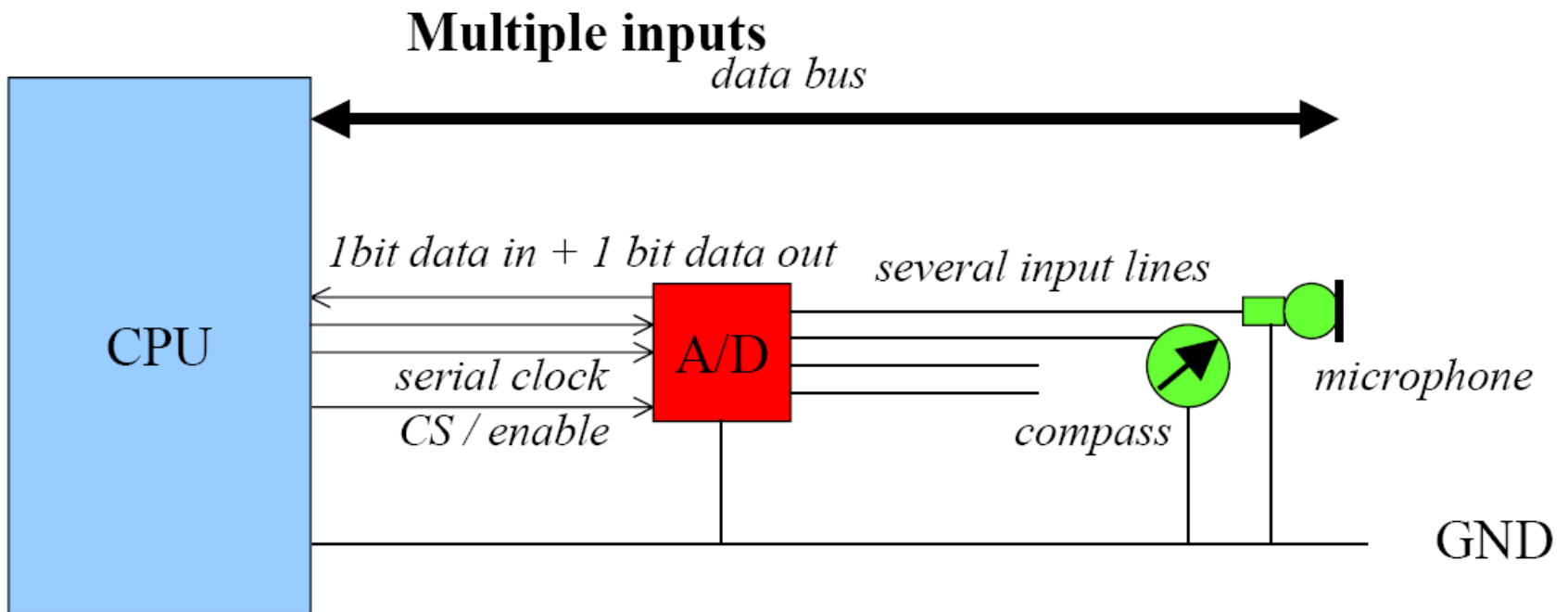

# A/D converter from MAXIM

19-0247; Rev. 0; 3/94

# MAXIM

## Low-Power, 8-Channel, Serial 10-Bit ADC

### General Description

The MAX192 is a low-cost, 10-bit data-acquisition system that combines an 8-channel multiplexer, high-bandwidth track/hold, and serial interface with high conversion speed and ultra-low power consumption. The device operates with a single +5V supply. The analog inputs are software configurable for single-ended and differential (unipolar/bipolar) operation.

The 4-wire serial interface connects directly to SPI™, QSPI™, and Microwire™ devices, without using external logic. A serial strobe output allows direct connection to TMS320 family digital signal processors. The MAX192 uses either the internal clock or an external serial-interface clock to perform successive approximation A/D conversions. The serial interface can operate beyond 4MHz when the internal clock is used. The MAX192 has an internal 4.096V reference with a drift of ±30ppm typical. A reference-buffer amplifier simplifies gain trim and two sub-LSBs reduce quantization errors.

The MAX192 provides a hardwired  $\overline{\text{SHDN}}$  pin and two software-selectable power-down modes. Accessing the serial interface automatically powers up the device, and the quick turn-on time allows the MAX192 to be shut down between conversions. By powering down between conversions, supply current can be cut to under 10µA at reduced sampling rates.

### Features

- ◆ 8-Channel Single-Ended or 4-Channel Differential Inputs
- ◆ Single +5V Operation
- ◆ Low Power: 1.5mA (operating)  
2µA (power-down)
- ◆ Internal Track/Hold, 133kHz Sampling Rate
- ◆ Internal 4.096V Reference
- ◆ 4-Wire Serial Interface is Compatible with SPI, QSPI, Microwire, and TMS320
- ◆ 20-Pin DIP, SO, SSOP Packages
- ◆ Pin-Compatible 12-Bit Upgrade (MAX186/MAX188)

### Ordering Information

PART	TEMP. RANGE	PIN-PACKAGE	INL(LSBs)
MAX192ACPP	0°C to +70°C	20 Plastic DIP	±1/2
MAX192BCPP	0°C to +70°C	20 Plastic DIP	±1
MAX192ACWP	0°C to +70°C	20 Wide SO	±1/2
MAX192BCWP	0°C to +70°C	20 Wide SO	±1
MAX192ACAP	0°C to +70°C	20 SSOP	±1/2
MAX192BCAP	0°C to +70°C	20 SSOP	±1
MAX192AEPP	-40°C to +85°C	20 Plastic DIP	±1/2
MAX192BEPP	-40°C to +85°C	20 Plastic DIP	±1
MAX192AEWP	-40°C to +85°C	20 Wide SO	±1/2
MAX192BEWP	-40°C to +85°C	20 Wide SO	±1

MAX192

# A/D converter


## Applications

Automotive  
Pen-Entry Systems  
Consumer Electronics  
Portable Data Logging  
Robotics  
Battery-Powered Instruments, Battery Management  
Medical Instruments

See last page for Typical Operating Circuit.

™ SPI and QSPI are trademarks of Motorola Corp.  
Microwire is a trademark of National Semiconductor Corp.

## Pin Configuration

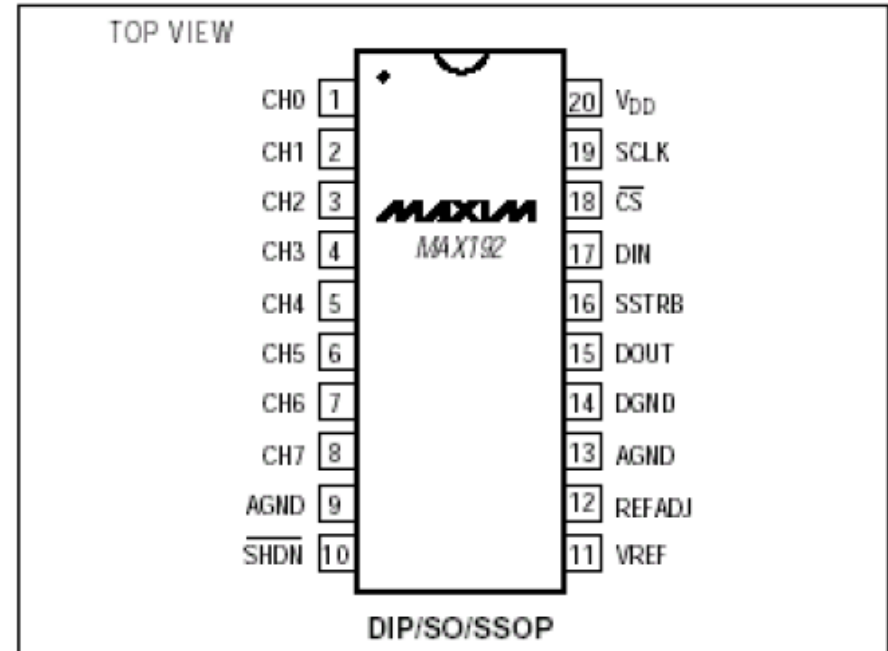



## ABSOLUTE MAXIMUM RATINGS

V <sub>DD</sub> to AGND	-0.3V to +6V
AGND to DGND	-0.3V to +0.3V
CH0-CH7 to AGND, DGND	-0.3V to (V <sub>DD</sub> + 0.3V)
VREF to AGND	-0.3V to (V <sub>DD</sub> + 0.3V)
REFADJ to AGND	-0.3V to (V <sub>DD</sub> + 0.3V)
Digital Inputs to DGND	-0.3V to (V <sub>DD</sub> + 0.3V)
Digital Outputs to DGND	-0.3V to (V <sub>DD</sub> + 0.3V)
Continuous Power Dissipation (T <sub>A</sub> = +70°C)	
Plastic DIP (derate 11.11mW/°C above +70°C)	889mW
SO (derate 10.00mW/°C above +70°C)	800mW

SSOP (derate 8.00mW/°C above +70°C)	640mW
CERDIP (derate 11.11mW/°C above +70°C)	889mW
Operating Temperature Ranges	
MAX192_C_P	0°C to +70°C
MAX192_E_P	-40°C to +85°C
MAX192_MJP	-55°C to +125°C
Storage Temperature Range	-60°C to +150°C
Lead Temperature (soldering, 10sec)	+300°C

Stresses beyond those listed under "Absolute Maximum Ratings" may cause permanent damage to the device. These are stress ratings only, and functional operation of the device at these or any other conditions beyond those indicated in the operational sections of the specifications is not implied. Exposure to absolute maximum rating conditions for extended periods may affect device reliability.

# A/D Converter

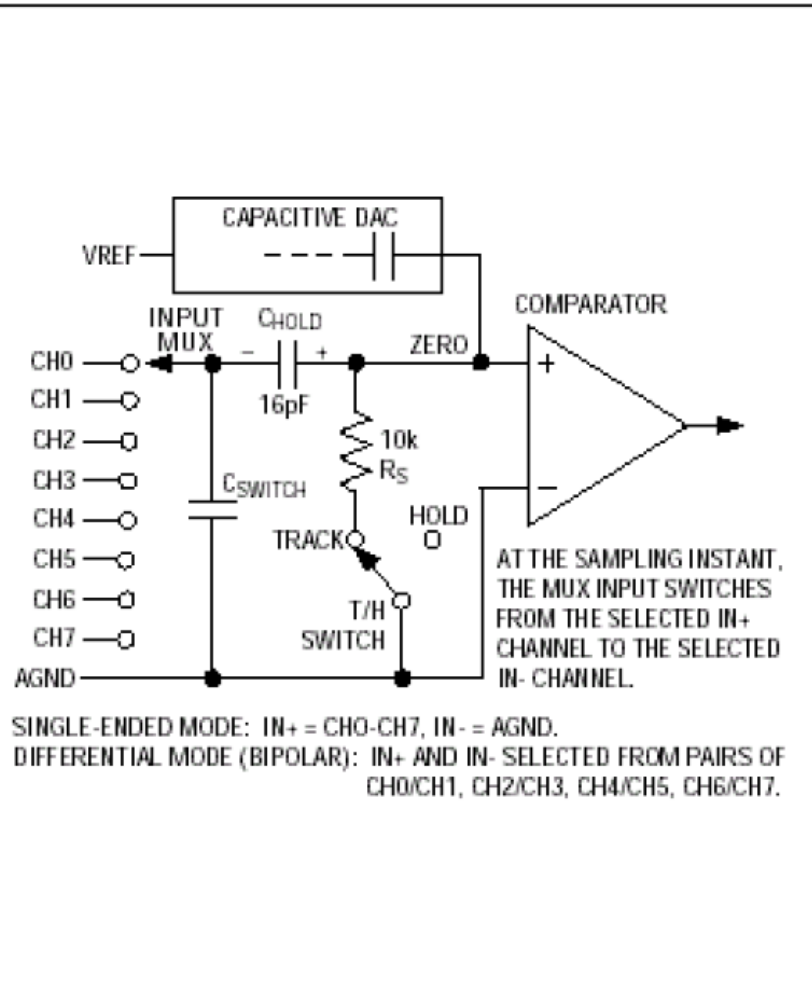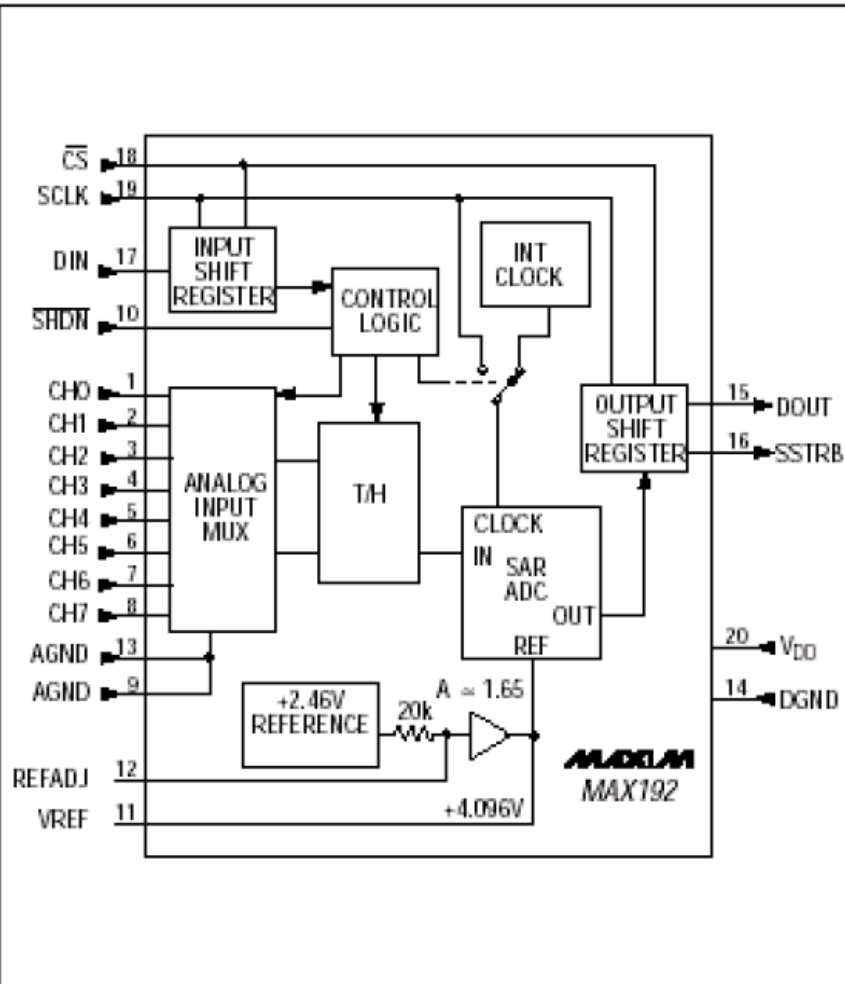


**MAX192**



# A/D Converter

MAX192

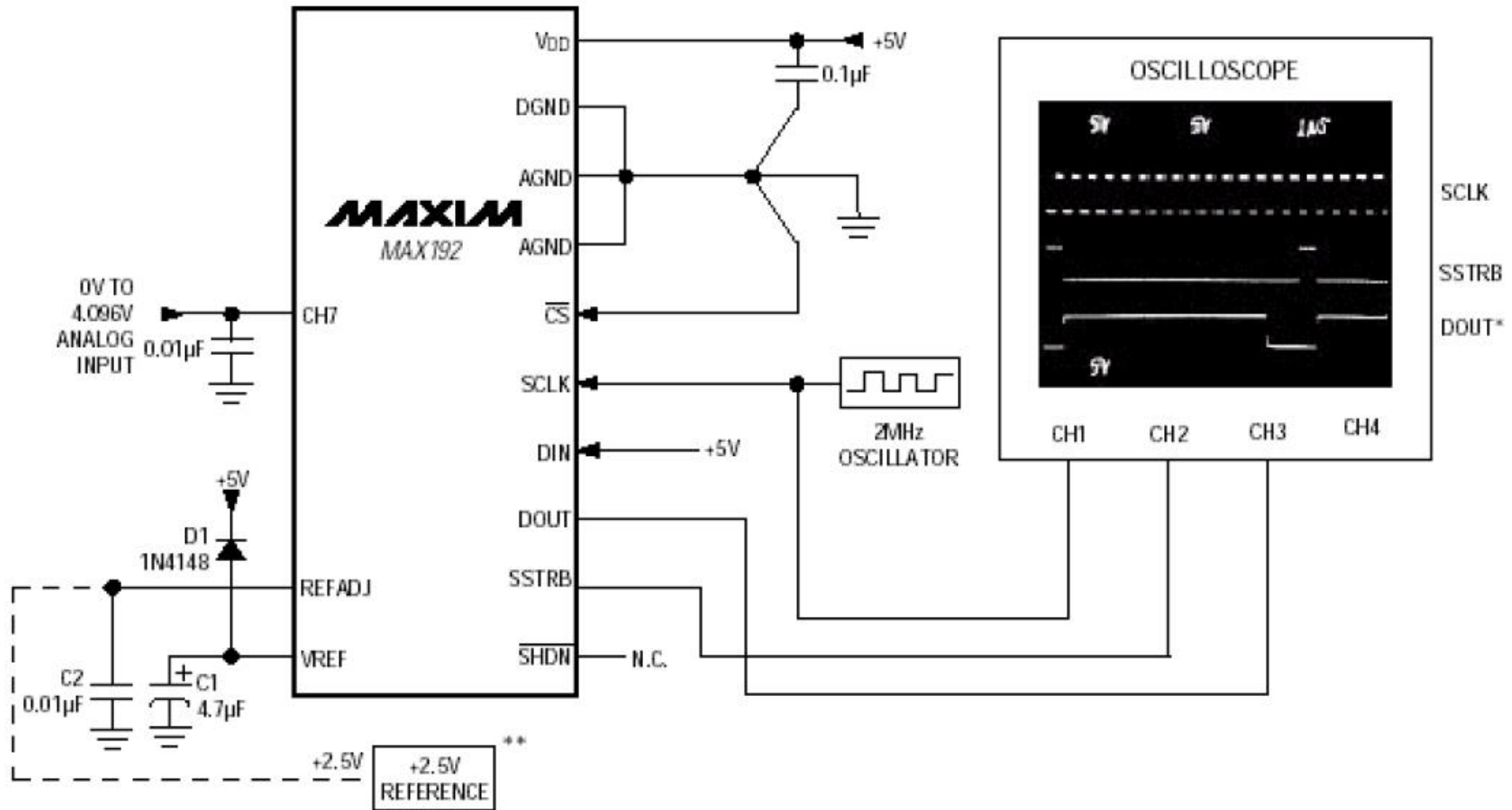


\* FULL-SCALE ANALOG INPUT, CONVERSION RESULT = \$FFF (HEX)

\*\*OPTIONAL. A POTENTIOMETER MAY BE USED IN PLACE OF THE REFERENCE FOR TEST PURPOSES.


# A/D Converter

## Serial clock and serial data stream

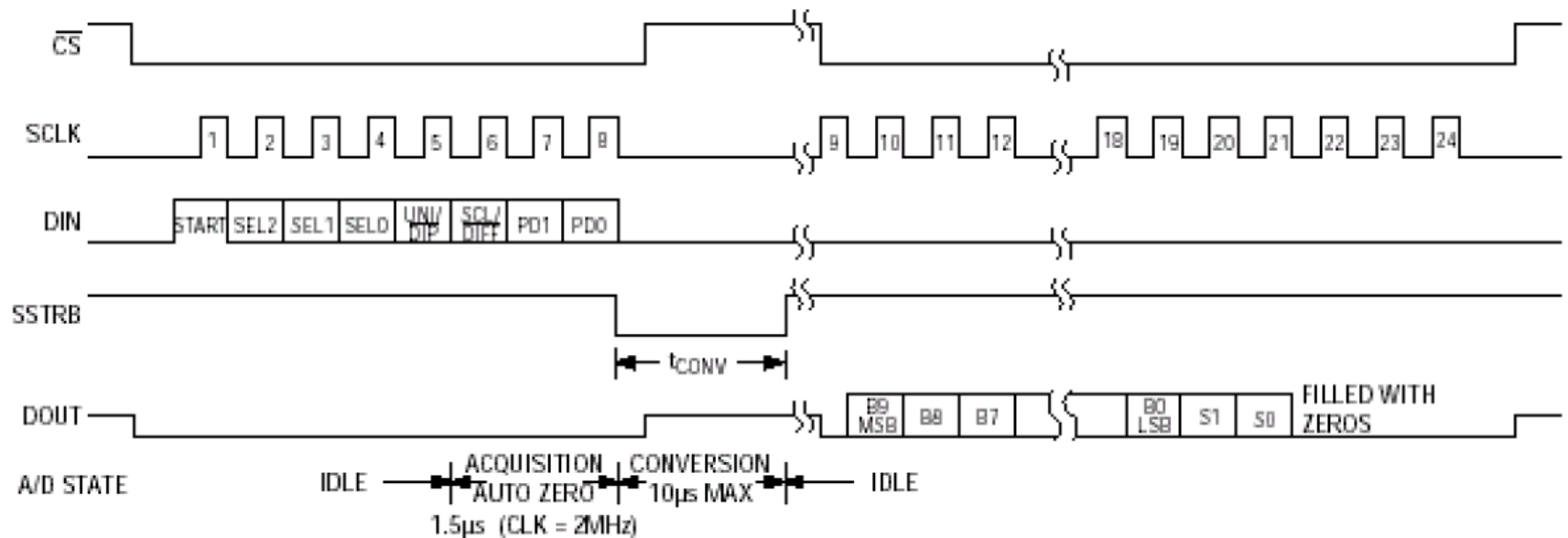


# A/D Converter

## Signal conversion


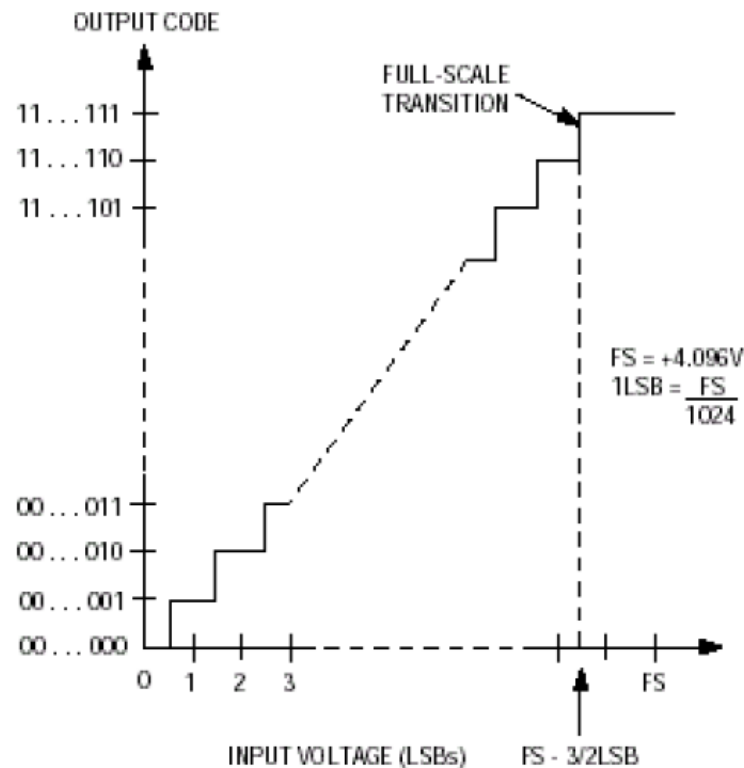


# A/D converter

## Power consumption

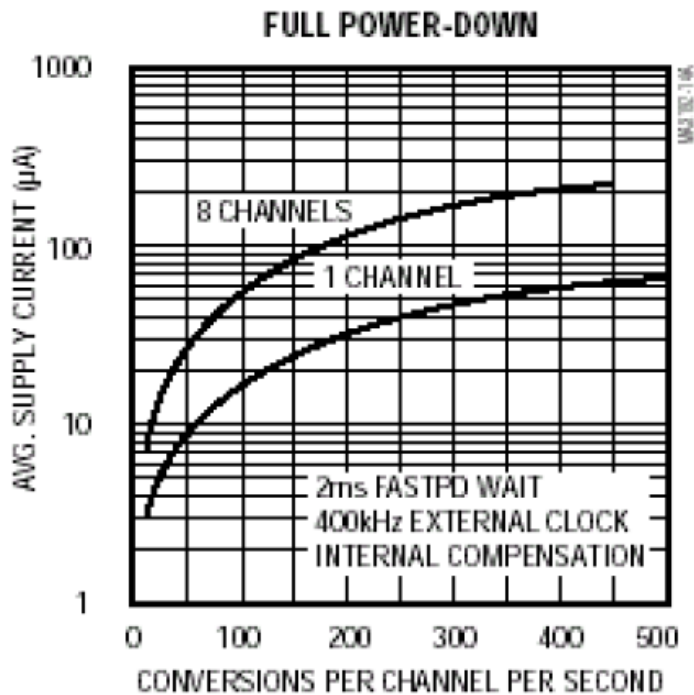

## Power-up delay

 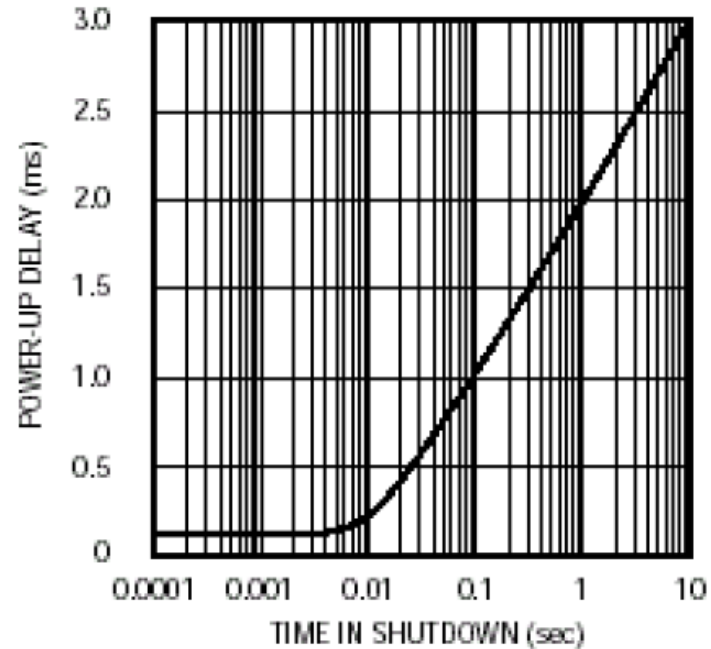

# Questions for students

1. Use of Ohm's Law and Voltage division in designing and adaptation of sensors.
2. Applications of pressure pads and potentiometers in robots. Discuss stationary and mobile robots.
3. Bend sensors and their uses.
4. A/D converters in robotics applications.
5. List applications of D/A converters.

# Sources

- ⌘ **T Brauni**
- ⌘ **A. Ferworn**
- ⌘ **Saúl J. Vega**
- ⌘ **Daisy A. Ortiz**
- ⌘ **Raúl E. Torres**
- ⌘ **Maja Mataric**
- ⌘ **Ali Emre Turgut**
- ⌘ **Dr. Linda Bushnell**
- ⌘ **Web Site: <http://www.ee.washington.edu/class/462/aut00/>**
- ⌘ **Robotic Explorations: A Hands-on Introduction to Engineering, Fred Martin, Prentice Hall, 2001.**