



Series and Parallel

How we wire the world

Series vs Parallel Circuits



Series Circuit

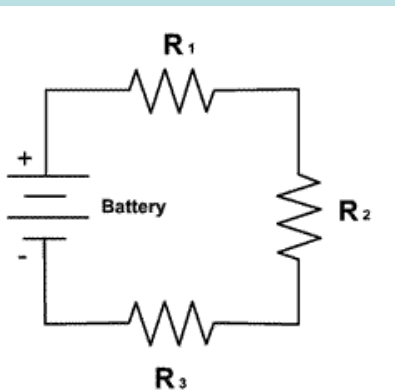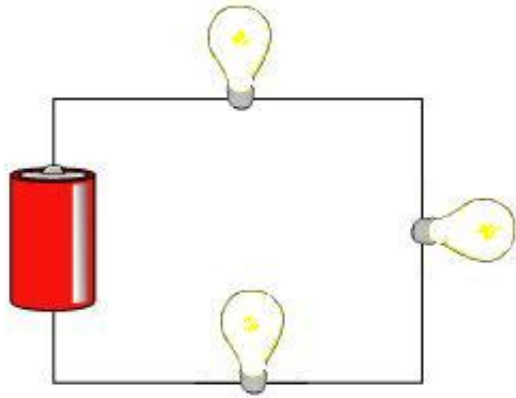- Electrons only have one path to flow through.




Parallel Circuit

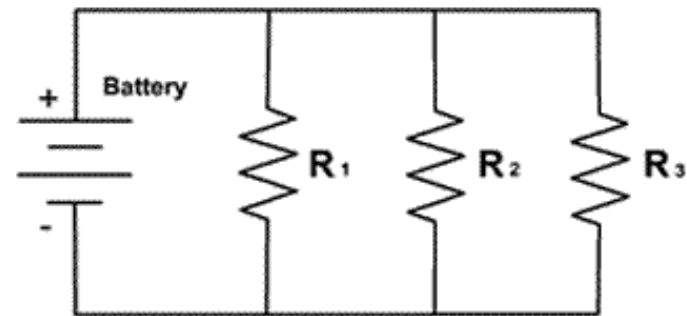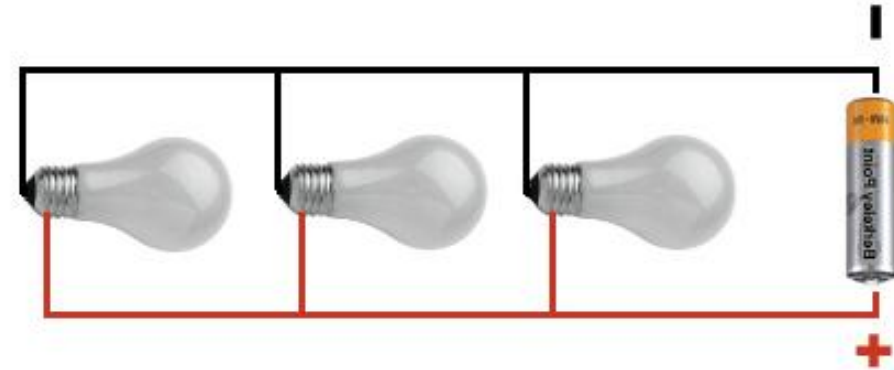- There are MULTIPLE paths for the current to flow through.



Series Circuit

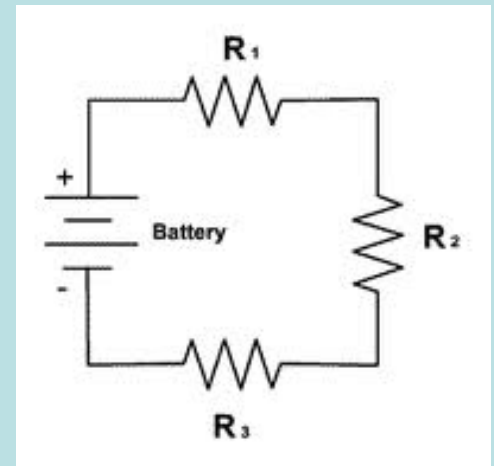- When electrons have to flow through one part to get to the next part




- More components = more resistance
- Increase resistance = decrease current (flow)
- Less current = less bright bulbs
- As voltage increases, current increases

Series Circuit – Pros & Cons

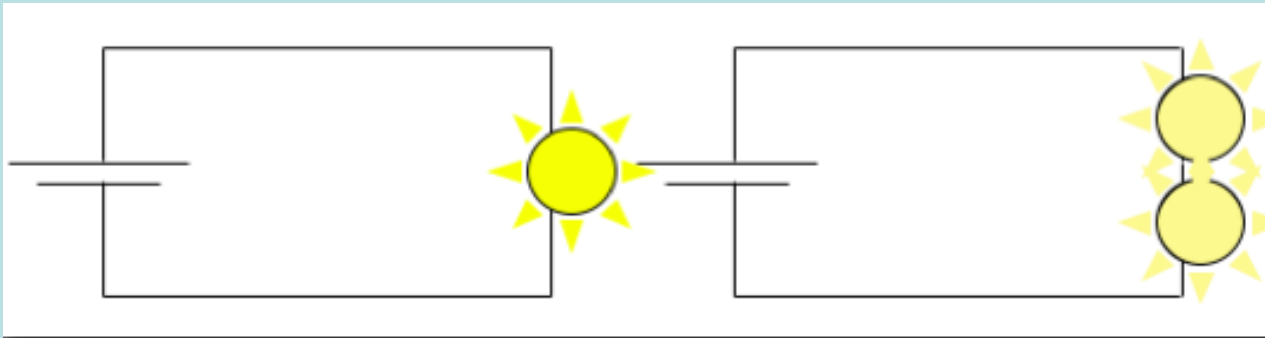Problems with Series:

- The more devices (resistors) in a series circuit, the less current passes through (dimmer bulbs).




- If one resistor breaks (a bulb goes out) the entire series is turned off.


Series Circuit - Resistance

- Resistors – resists the flow of electrical current
- Increased resistance will reduce the rate at which charge flows (aka current)
- Total resistance goes UP with each resistor since the current has must go through each resistor.
- Total Resistance = Sum of all resistors in the series


$$R_{eq} = R_1 + R_2 + R_3 \dots$$

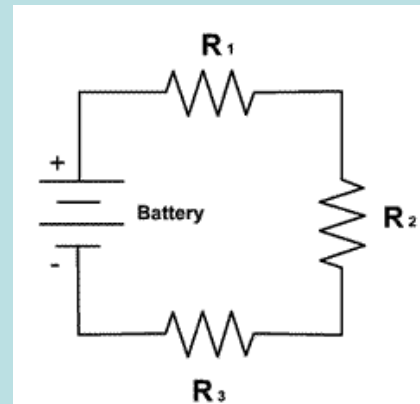

Series Circuit - Current

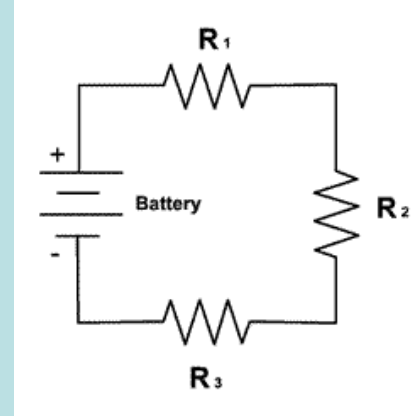

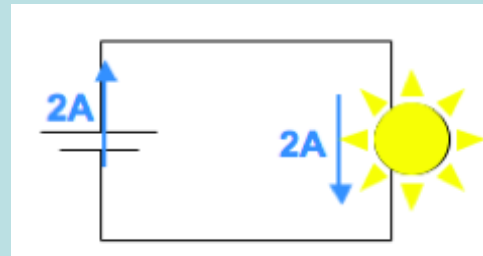- Current = amount of charge (flow of electrons)
 - Like the flow of water
- A current can't just disappear (appear)
 - Since only one path if some electrons flow through R1, then they have to continue flowing through R2 and R3.




- Since the Current is the same through the entire circuit
- $$I_T = I_1 = I_2 = I_3$$

Series Circuit - Voltage

- Voltage is the electric equivalent of water pressure.
 - The higher the voltage, the faster electrons will flow through the conductor.
- Each component has resistance that causes a drop in voltage (reduction in voltage).
- Total Voltage = The sum of voltages across each series resistors

$$V_T = V_1 + V_2 + V_3 \dots$$

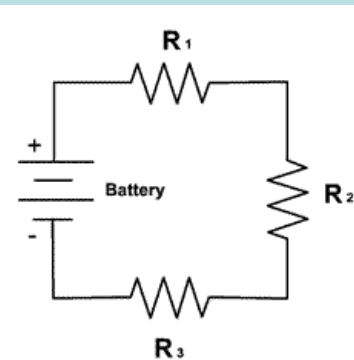

Series vs Parallel Chart

	Series	Parallel
Voltage (V)	$V_{\text{tot}} = V_1 + V_2 + V_3 \dots$	
Current (I)	$I_{\text{tot}} = I_1 = I_2 = I_3$	
Resistance (R)	$R_{\text{eq}} = R_1 + R_2 + R_3 \dots$	


Series Circuit - Example

- Given

- $V_{\text{battery}} = 12 \text{ V}$

- $R_1 = 50 \text{ } \Omega$, $R_2 = 100 \text{ } \Omega$, $R_3 = 100 \text{ } \Omega$

- **Complete the following table**

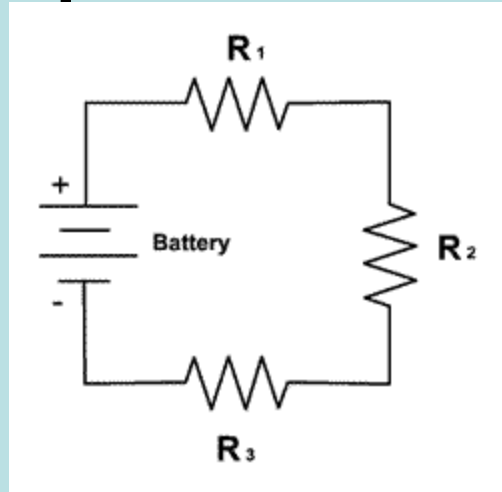

V	=	I	R
---	---	---	---

1			
---	--	--	--

2			
---	--	--	--

3			
---	--	--	--

-------	--	--	--

T			
---	--	--	--

Parallel Circuit – Pros and Cons

Advantages

- The more devices (resistors) in a parallel circuit, does not decrease the current (does not dim bulbs).
- If one resistor breaks (a bulb goes out) the rest do not.

Problems

- Current doesn't stay the same for entire circuit
 - So energy is used up quicker
 - So the total current increases = faster electrons = hotter wire = fire?

Which is better? Series or Parallel?

Parallel

- Most things are wired in parallel
- Because of the fact that the more you plug in, the intensity doesn't decrease.
- Of course, this also increases the risk of fire
- This is why homes have fuses or circuit breakers. They turn off everything in the circuit when current moves too fast.

TOLL BOOTH EXPLANATION


- Adding toll booths in series increases resistance and slows the current flow.
- Adding toll booths in parallel lowers resistance and increases the current flow.

Parallel Circuit - Resistance

- Resistors added side-by-side
- The more paths, the less TOTAL resistance.

$$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$$


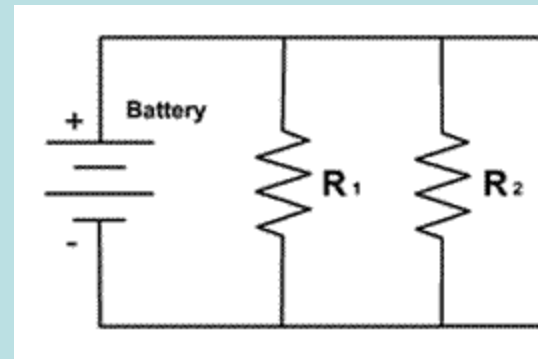
- Ex. 2 resistors in parallel with 4Ω each.
 - Since the circuit offers two *equal* pathways for charge flow, only $1/2$ the charge will *choose* to pass through a given branch.



Parallel Circuit - Current

- ALL paths are used!
 - But the charge *divides* up into all branches
 - One branch can have more current than another branch (depends on resistance in branch).
- Total current = sum of current in each path


$$I_T = I_1 + I_2 + \dots$$

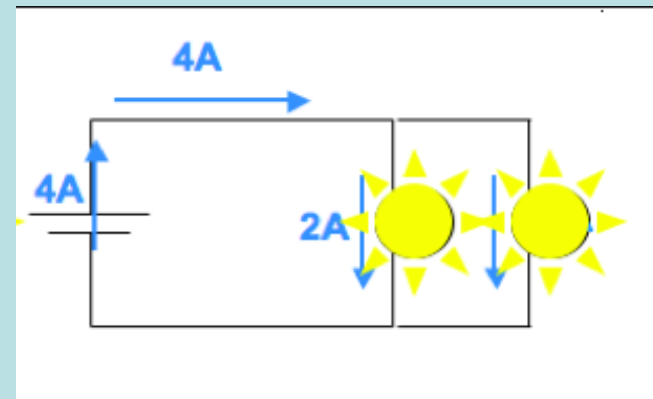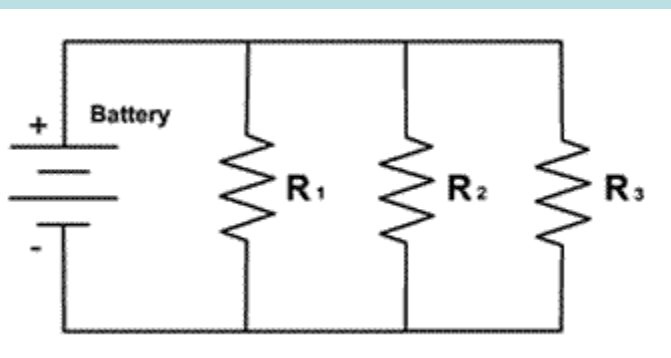

Parallel Circuit - Voltage

- A charge only passes through a single resistor.
- Voltage drop across the resistor that it *chooses* to pass through must equal the voltage of the battery.
- Total voltage = the voltage across each individual resistor


$$V_T = V_1 = V_2 = \dots$$

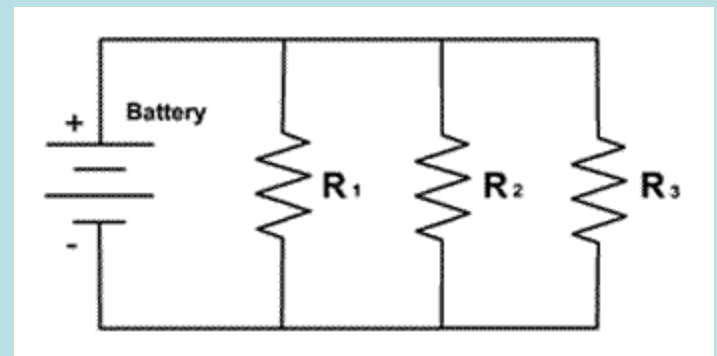

Series vs Parallel Chart

	Series	Parallel
Voltage (V)	$V_{\text{tot}} = V_1 + V_2 + V_3 \dots$	$V_{\text{tot}} = V_1 = V_2 = \dots$
Current (I)	$I_{\text{tot}} = I_1 = I_2 = I_3$	$I_{\text{tot}} = I_1 + I_2 + \dots$
Resistance (R)	$R_{\text{eq}} = R_1 + R_2 + R_3 \dots$	$1/R_{\text{eq}} = 1/R_1 + 1/R_2 + 1/R_3$

Parallel Circuit - Example

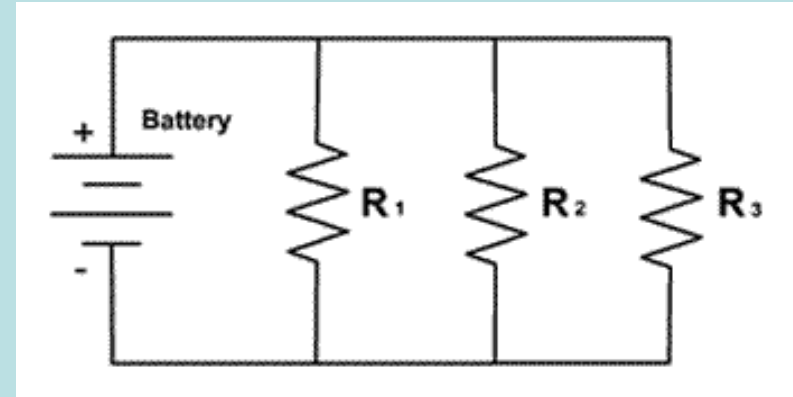

- **Given**

- $V_{\text{battery}} = 12 \text{ V}$

- $R_1 = 50 \Omega, R_2 = 100 \Omega, R_3 = 100 \Omega$

- **Complete the following table:**

V	=	I	R
---	---	---	---

1			
---	--	--	--

2			
---	--	--	--

3			
---	--	--	--

T			
---	--	--	--

Two Types of Current

- **DC—Direct Current**
 - produced by solar cells and chemical cells (batteries)
 - Current only flows in one direction.
- **AC—Alternating Current**
 - Current flows back and forth (alternates)
 - Found in homes
 - Generators produce AC current